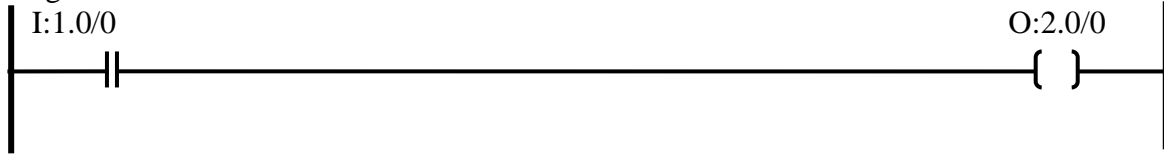



LECTURE - 4

ALLEN BRADLEY PLC SLC 5/03


Simple Logic




NOT Gate

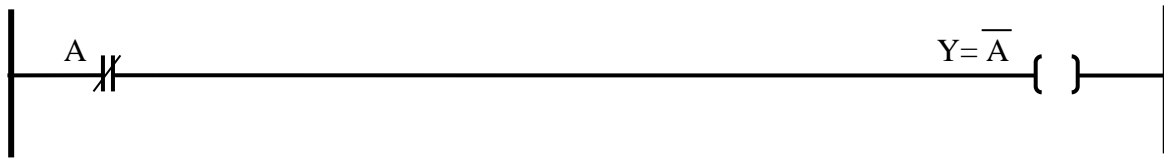


OR / NAND Gate

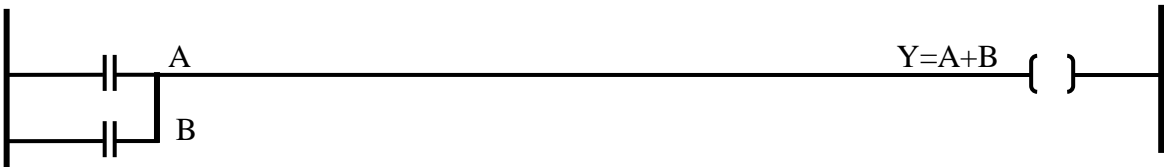


AND / NOR Gate

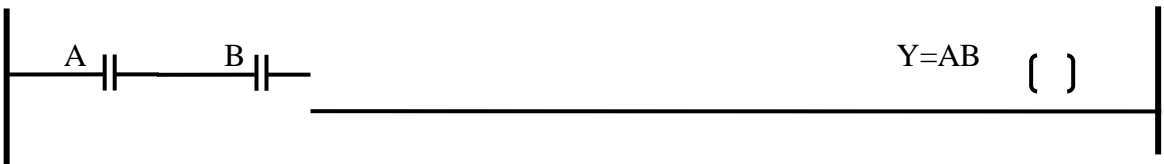

EX-OR Gate

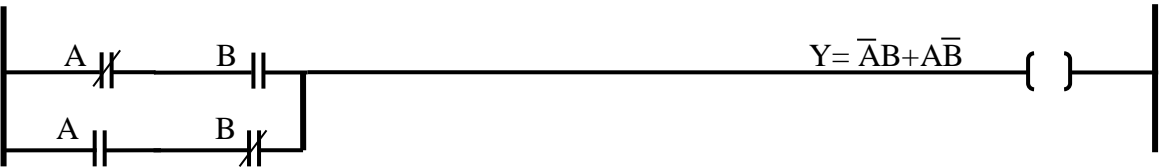


EX-NOR Gate

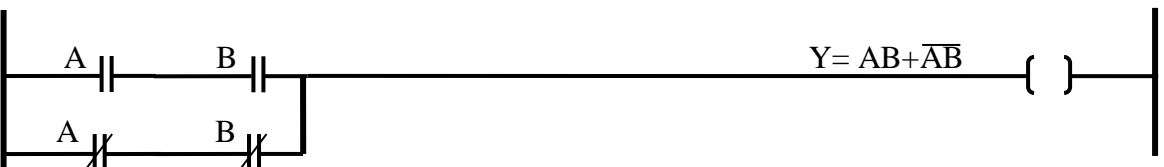

Latch / Unlatch

One type

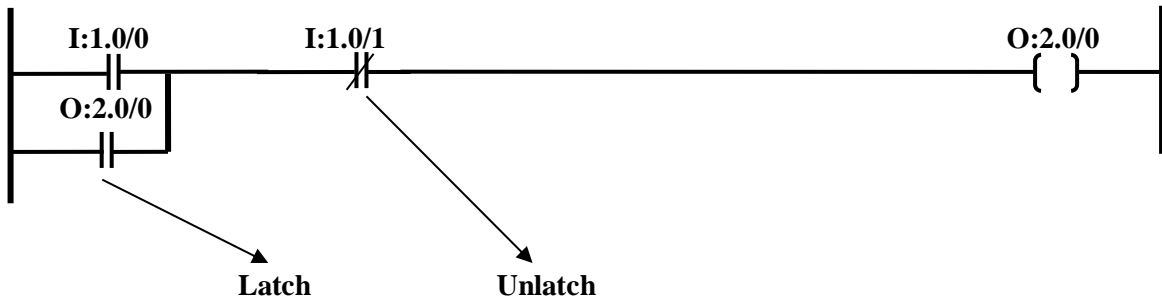

Another type

