
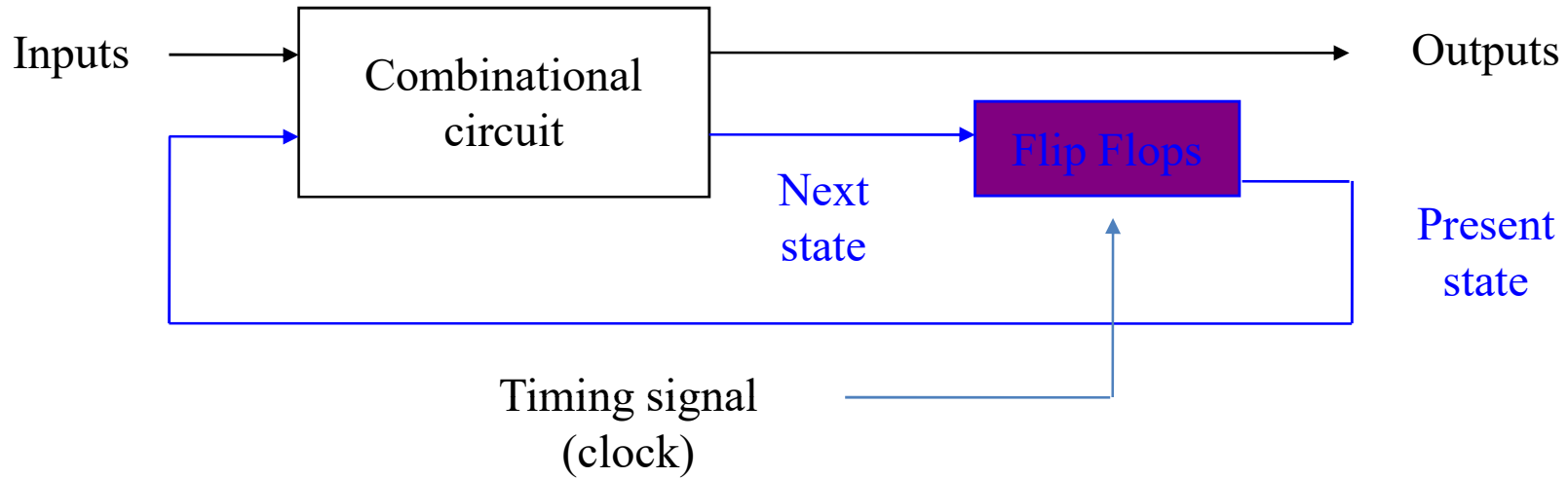


# **Sequential Circuit(D-Latch & D-Flip Flop)**

# Sequential Circuits

 


Clock  
a periodic external event (input)




synchronizes when current state changes happen  
keeps system well-behaved  
makes it easier to design and build large systems

## Cross-coupled Inverters

A stable value can be stored at inverter outputs

 


State 1

 

State 2
 
## D Latch


$Q_0$  indicates the **previous state** (the previously stored value)



D	C	Q	Q'
0	1	0	1
1	1	1	0
X	0	$Q_0$	$Q_0'$

X	Y	C	Q	Q'
0	0	1	$Q_0$	$Q_0'$ Store
0	1	1	0	1 Reset
1	0	1	1	0 Set
1	1	1	1	1 Disallowed
X	X	0	$Q_0$	$Q_0'$ Store


## D Latch

 


D	C	Q	Q'
0	1	0	1
1	1	1	0
X	0	$Q_0$	$Q_0'$

Input value  $D$  is passed to output  $Q$  when  $C$  is high  
Input value  $D$  is ignored when  $C$  is low

## D Latch


 


Latches on following  
edge of clock

 


Z only changes when E is high  
If E is high, Z will follow X

## D Latch

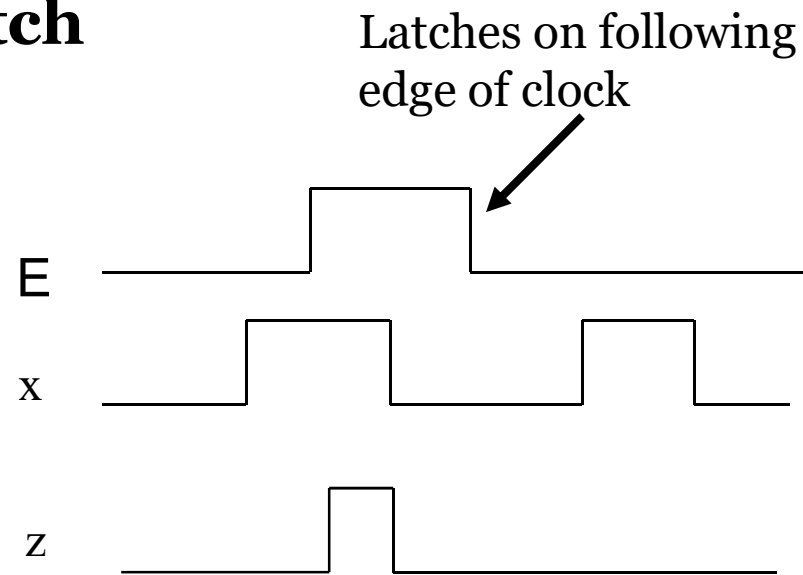 

The **D latch** stores data indefinitely, regardless of input D values, if  $C = 0$   
Forms basic storage element in computers

## Symbols for Latches

 

SR latch is based on NOR gates

S'R' latch based on NAND gates

D latch can be based on either.

D latch sometimes called transparent latch




## Summary

- With additional gates, an S-R latch can be converted to a D latch (**D** stands for **data**)
- D latch is simple to understand conceptually
  - When **C = 1**, data input **D** stored in latch and output as **Q**
  - When **C = 0**, data input **D** ignored and previous latch value output at **Q**

## Overview

- Latches respond to trigger **levels** on control inputs
  - **Example: If  $G = 1$ , input reflected at output**
- Difficult to precisely time when to store data with latches
- **Flip flips** store data on a **rising** or **falling** trigger edge.
  - Example: control input transitions from 0 -> 1, data input appears at output
  - Data remains stable in the flip flop until until next rising edge.
- Different types of flip flops serve different functions
- Flip flops can be defined with **characteristic functions**.

## D Latch

 

D	C	Q	Q'
0	1	0	1
1	1	1	0
X	0	Q <sub>0</sub>	Q <sub>0</sub> '


S	R	C	Q	Q'	
0	0	1	Q <sub>0</sub>	Q <sub>0</sub> '	Store
0	1	1	0	1	Reset
1	0	1	1	0	Set
1	1	1	1	1	Disallowed
X	X	0	Q <sub>0</sub>	Q <sub>0</sub> '	Store

When C is high, D passes from input to output (Q)


# Clocking Event

What if the output only changed on a C **transition**?


Positive edge triggered

 

D	C	Q	Q'
0	↑	0	1
1	↑	1	0
X	0	Q <sub>0</sub>	Q <sub>0</sub> '

 


Hi-Lo edge

 

Lo-Hi edge
 
## Master-Slave D Flip Flop

Consider two latches combined together  
Only one  $C$  value active at a time  
Output changes on **falling** edge of the clock




## D Flip-Flop

Stores a value on the positive edge of  $C$

Input changes at other times have no effect on output

Positive edge triggered

 


D	C	Q	Q'
0	↑	0	1
1	↑	1	0
X	0	Q <sub>0</sub>	Q <sub>0</sub> '

D gets latched to Q on the rising edge of the clock.
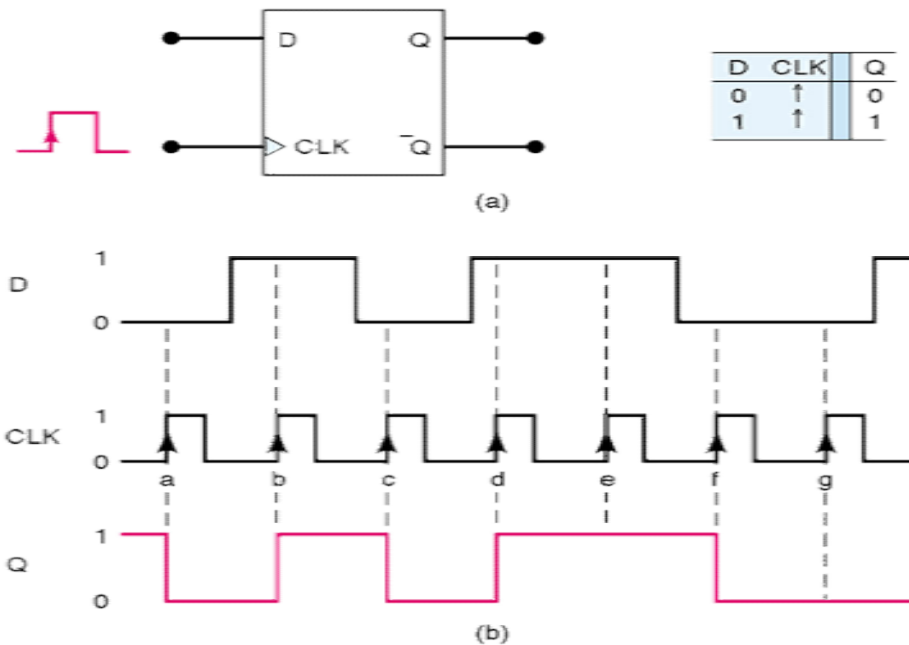
## Clocked D Flip-Flop

Stores a value on the positive edge of  $C$


Input changes at other times have no effect on output


 
## Positive and Negative Edge D Flip-Flop

D flops can be triggered on positive or negative edge


Bubble before *Clock (C)* input indicates **negative edge trigger**



(a) Positive edge



Lo-Hi edge

 

(a) Negati



Hi-Lo edge



## Summary

- Flip flops are powerful storage elements
  - They can be constructed from gates and latches!
- D flip flop is simplest and most widely used
- Asynchronous inputs allow for clearing and presetting the flip flop output
- Multiple flops allow for data storage
  - The basis of computer memory!
- Combine storage and logic to make a computation circuit

THANK YOU