


Sequential Circuit (Register)

Introduction: Registers

- An *n-bit register* has a group of n flip-flops and some logic gates and is capable of storing n bits of information.
- The flip-flops store the information while the gates control when and how new information is transferred into the register.
- Some functions of register:
 - ❖ retrieve data from register
 - ❖ store/load new data into register (serial or parallel)
 - ❖ shift the data within register (left or right)

Simple Registers

 
- No external gates.
- Example: A 4-bit register. A new 4-bit data is loaded every clock cycle.



Registers With Parallel Load


- Instead of loading the register at every clock pulse, we may want to control when to load.
- *Loading* a register: transfer new information into the register. Requires a *load* control input.
- *Parallel loading*: all bits are loaded simultaneously.

Registers With Parallel Load

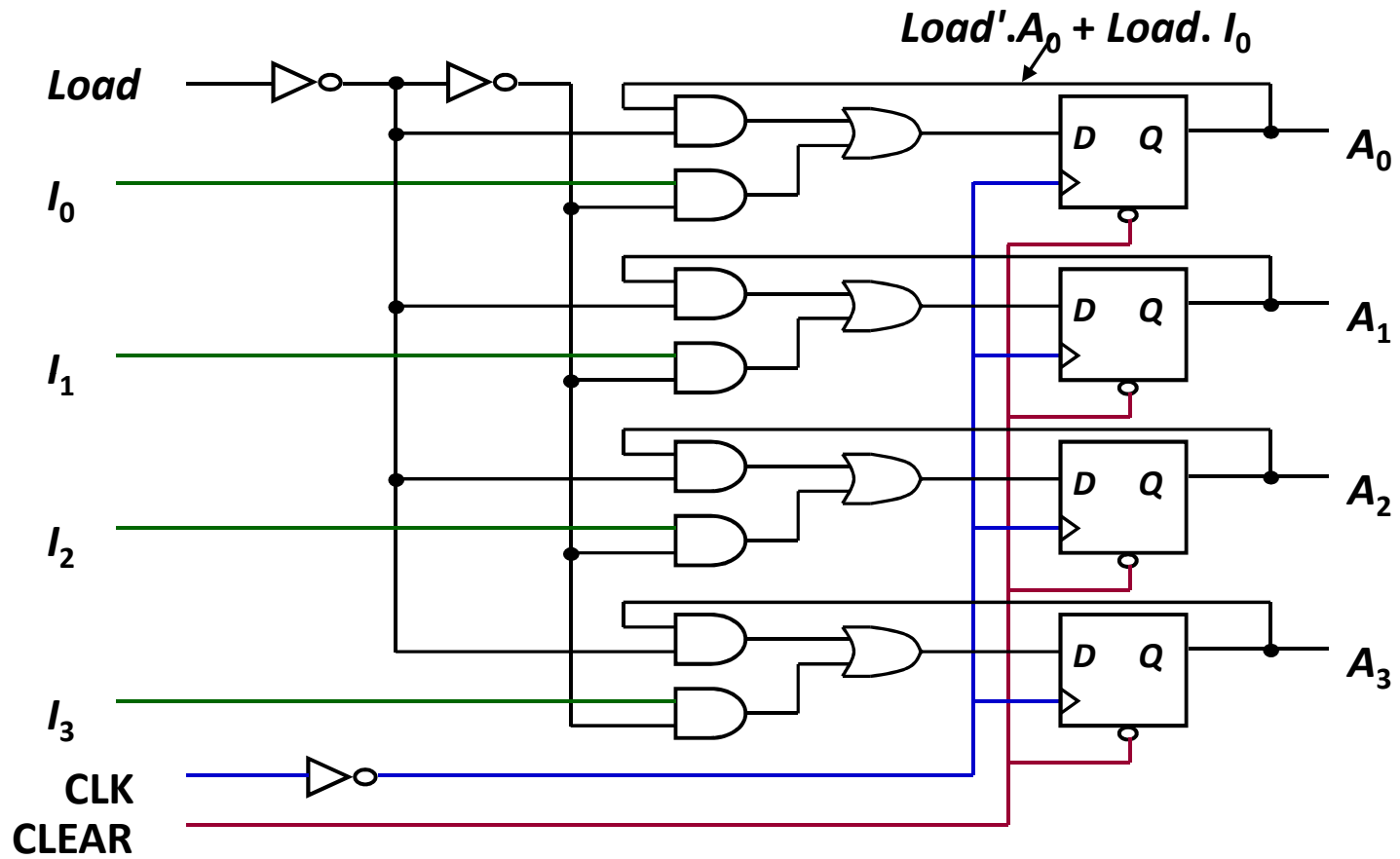

Using Registers to implement Sequential Circuits

 - A sequential circuit may consist of a *register* (memory) and a *combinational circuit*.



- The external inputs and present states of the register determine the next states of the register and the external outputs, through the combinational circuit.
- The combinational circuit may be implemented by any of the methods covered in *MSI components* and *Programmable Logic Devices*.

Cont...


- Example 1:

$$A_1^+ = \sum m(4,6) = A_1 \cdot x'$$

$$A_2^+ = \sum m(1,2,5,6) = A_2 \cdot x' + A_2' \cdot x = A_2 \oplus x$$

$$y = \sum m(3,7) = A_2 \cdot x$$

Present state		Input x	Next State		Output y
A_1	A_2		A_1^+	A_2^+	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

 


Cont...

- Example 2: Repeat example 1, but use a ROM.

Address			Outputs		
1	2	3	1	2	3
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	0	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	0	0	1

ROM truth table

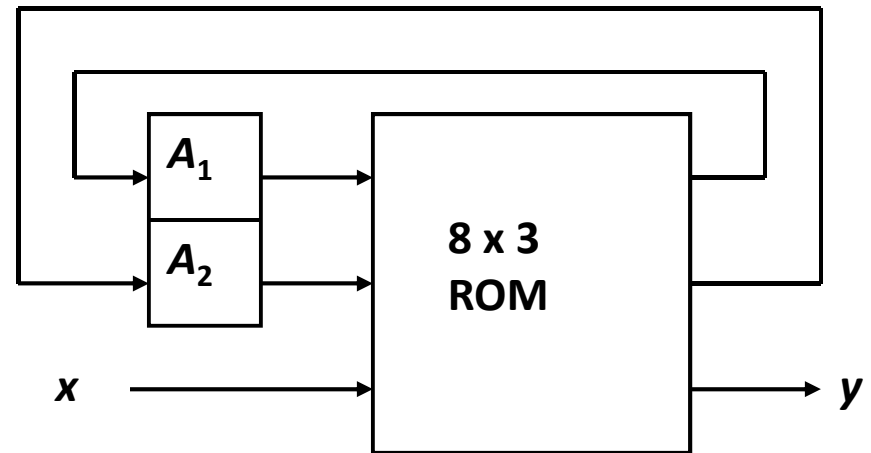


Shift Registers


- Another function of a register, besides storage, is to provide for *data movements*.
- Each *stage* (flip-flop) in a shift register represents one bit of storage, and the shifting capability of a register permits the movement of data from stage to stage within the register, or into or out of the register upon application of clock pulses.

Cont...

 
- Basic data movement in shift registers (four bits are used for illustration).




(a) Serial in/shift right/serial out

 


(b) Serial in/shift left/serial out

 


(c) Parallel in/serial out

 


(d) Serial in/parallel out

 

(e) Parallel in / parallel out

 


(f) Rotate right

 

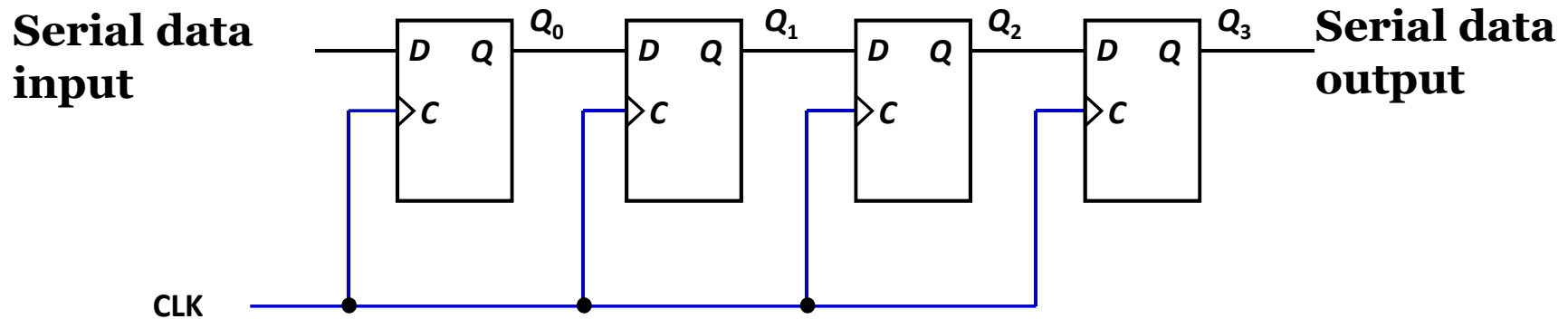(g) Rotate left


Serial In/Serial Out Shift Registers

- Accepts data serially – one bit at a time – and also produces output serially.



Serial In/Serial Out Shift Registers

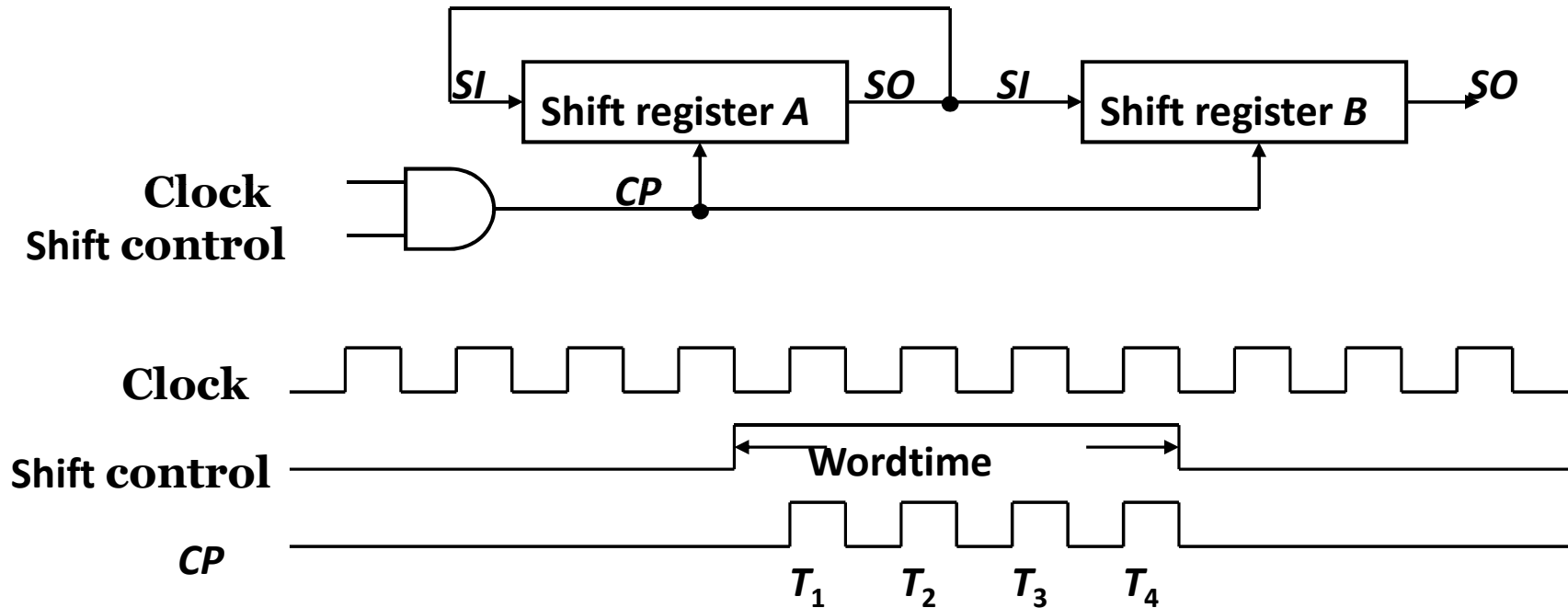- Application: Serial transfer of data from one register to another.



Serial In/Serial Out Shift Registers

- Serial-transfer example.

Timing Pulse	Shift register A	Shift register B	Serial output of B
Initial value	1 0 1 1	0 0 1 0	0
After T_1	1 1 0 1	1 0 0 1	1
After T_2	1 1 1 0	1 1 0 0	0
After T_3	0 1 1 1	0 1 1 0	0
After T_4	1 0 1 1	1 0 1 1	1

Serial In/Parallel Out Shift Registers

- Accepts data serially.
- Outputs of all stages are available simultaneously.

