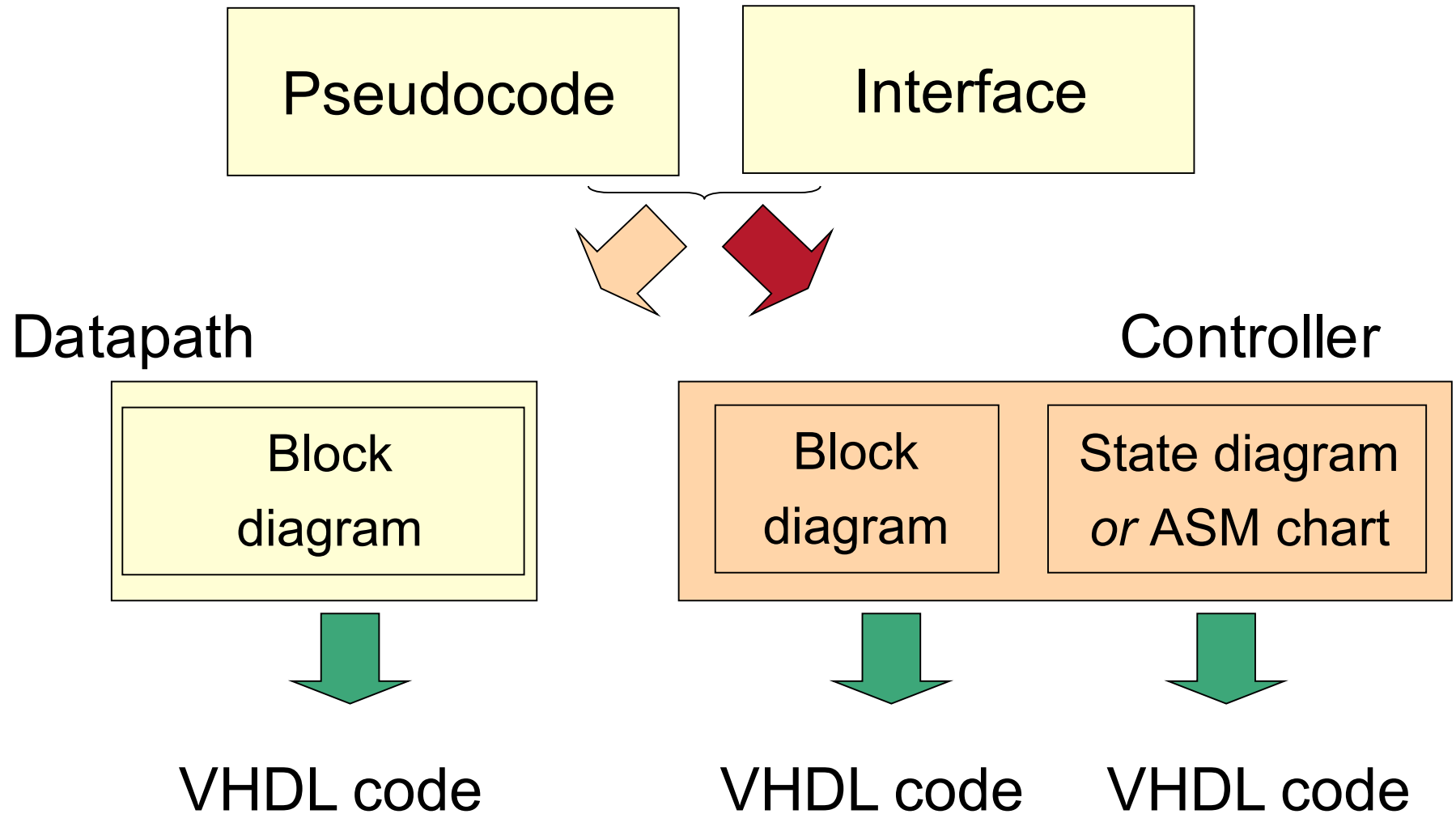


Finite State Machines

- Digital Systems and especially their Controllers can be described as Finite State Machines (FSMs)
- Finite State Machines can be represented using
 - **State Diagrams and State Tables** - suitable for simple digital systems with a relatively few inputs and outputs
 - **Algorithmic State Machine (ASM) Charts** - suitable for complex digital systems with a large number of inputs and outputs
- All these descriptions can be easily translated to the corresponding synthesizable VHDL code

Hardware Design with RTL VHDL



Steps of the Design Process

1. Text description
2. Interface
3. Pseudocode
4. Block diagram of the Datapath
5. Interface with the division into the Datapath and the Controller
6. ASM chart of the Controller
7. RTL VHDL code of the Datapath, the Controller, and the Top Unit
8. Testbench of the Datapath, the Controller, and the Top Unit
9. Functional simulation and debugging
10. Synthesis and post-synthesis simulation
11. Implementation and timing simulation
12. Experimental testing

Steps of the Design Process Practiced in Class Today

1. Text description
2. Interface
3. Pseudocode
4. Block diagram of the Datapath
5. Interface with the division into the Datapath and the Controller
- 6. ASM chart of the Controller**
- 7. RTL VHDL code of the Datapath, the Controller, and the Top Unit**
- 8. Testbench of the Datapath, the Controller, and the Top Unit**
9. Functional simulation and debugging
10. Synthesis and post-synthesis simulation
11. Implementation and timing simulation
12. Experimental testing




Finite State Machines Refresher

Finite State Machines (FSMs)

- Any Circuit with Memory Is a Finite State Machine
 - Even computers can be viewed as huge FSMs
- Design of FSMs Involves
 - Defining states
 - Defining transitions between states
 - Optimization / minimization
- Manual Optimization/Minimization Is Practical for Small FSMs Only


Moore FSM

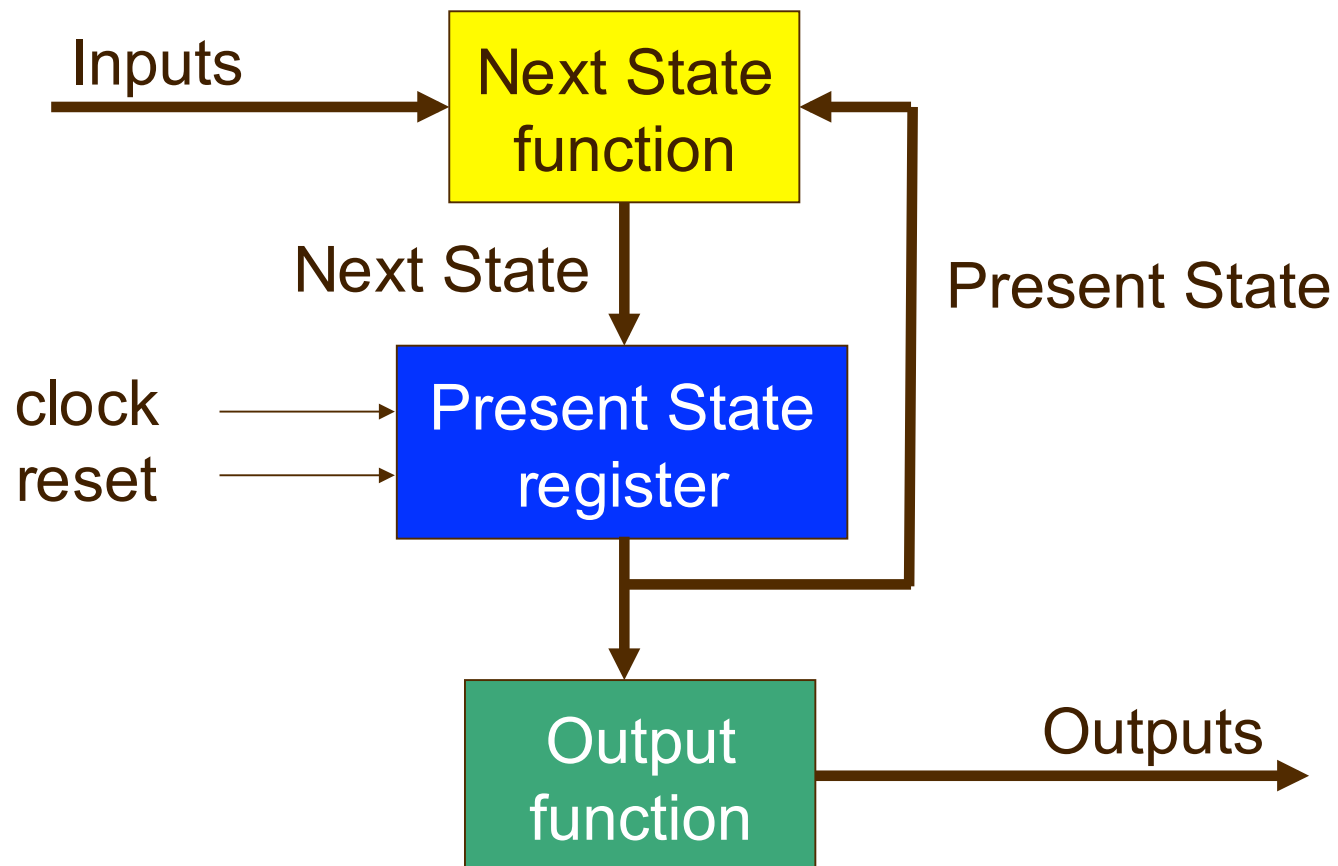- Output Is a Function of a Present State Only



Mealy FSM

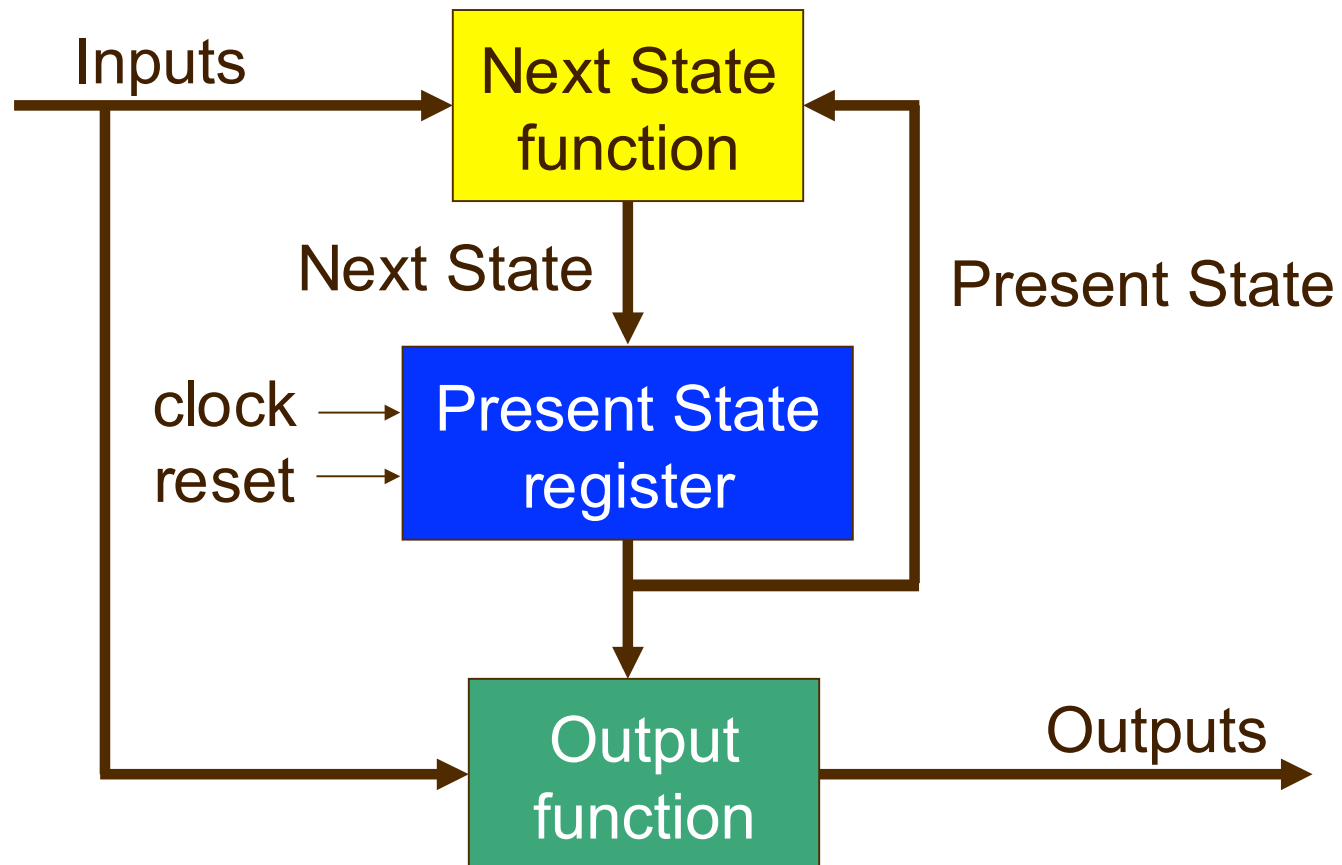
- Output Is a Function of a Present State and Inputs




The image features a central Xilinx chip with the logo and name 'XILINX' visible. Surrounding the chip are several circular icons representing different applications: a server rack, a laptop, a mobile phone, a keyboard, and a printer. The background is a light blue grid with the words 'High Performance' and 'Low Power' written in a stylized font. The overall theme is digital technology and embedded systems.

State Diagrams

Moore Machine

 

Mealy Machine

 

Moore vs. Mealy FSM (1)


- Moore and Mealy FSMs Can Be Functionally Equivalent
 - Equivalent Mealy FSM can be derived from Moore FSM and vice versa
- Mealy FSM Has Richer Description and Usually Requires Smaller Number of States
 - Smaller circuit area

Moore vs. Mealy FSM (2)

- Mealy FSM Computes Outputs as soon as Inputs Change
 - Mealy FSM responds one clock cycle sooner than equivalent Moore FSM
- Moore FSM Has No Combinational Path Between Inputs and Outputs
 - Moore FSM is less likely to affect the critical path of the entire circuit

Moore FSM - Example 1

 
- Moore FSM that Recognizes Sequence "10"



| | | | |
|-----------------------|--|---------------------|----------------------|
| Meaning of states: | S0: No elements of the sequence observed | S1: "1" observed | S2: "10" observed |
|-----------------------|--|---------------------|----------------------|

Mealy FSM - Example 1

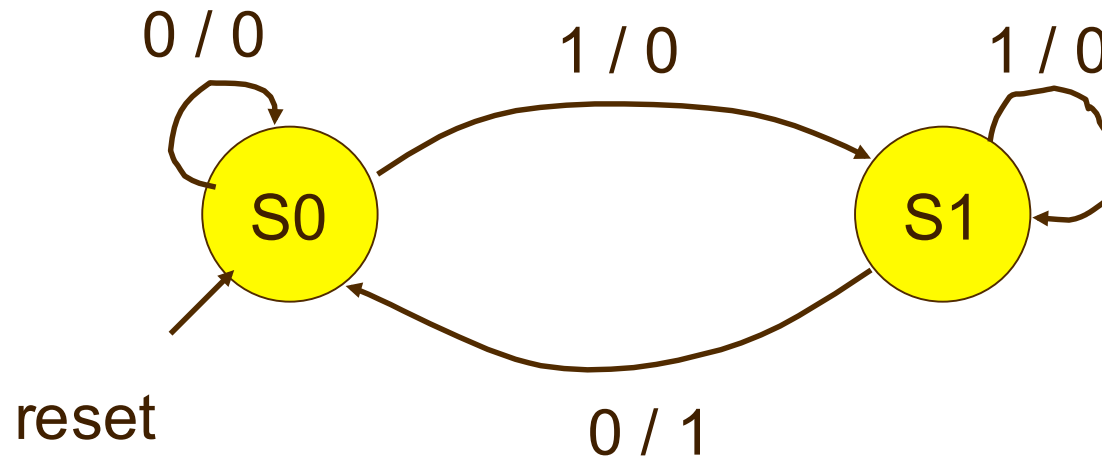- Mealy FSM that Recognizes Sequence "10"




Meaning
of states:

S0: No
elements
of the
sequence
observed

S1: "1"
observed

Moore & Mealy FSMs – Example 1

 

The image features a central microchip with the text 'CoolRunner-II' on its surface. Surrounding the chip are several circular icons: a multi-pin connector, a multi-pin connector, a keyboard, a mouse, a mobile phone, and a small electronic component. The background is a light blue grid with various text labels in a stylized font: 'High Performance' (top left), 'Low Power' (bottom left), 'CoolClock' (top right), and 'CoolCache' (bottom right).


Finite State Machines in VHDL

FSMs in VHDL

- Finite State Machines Can Be Easily Described With Processes
- Synthesis Tools Understand FSM Description if Certain Rules Are Followed
 - **State transitions** should be described **in a process** sensitive to *clock* and *asynchronous reset* signals **only**
 - **Output function** described using rules for combinational logic, i.e. as **concurrent statements** or a **process with all inputs in the sensitivity list**


Moore FSM

process(clock, reset)

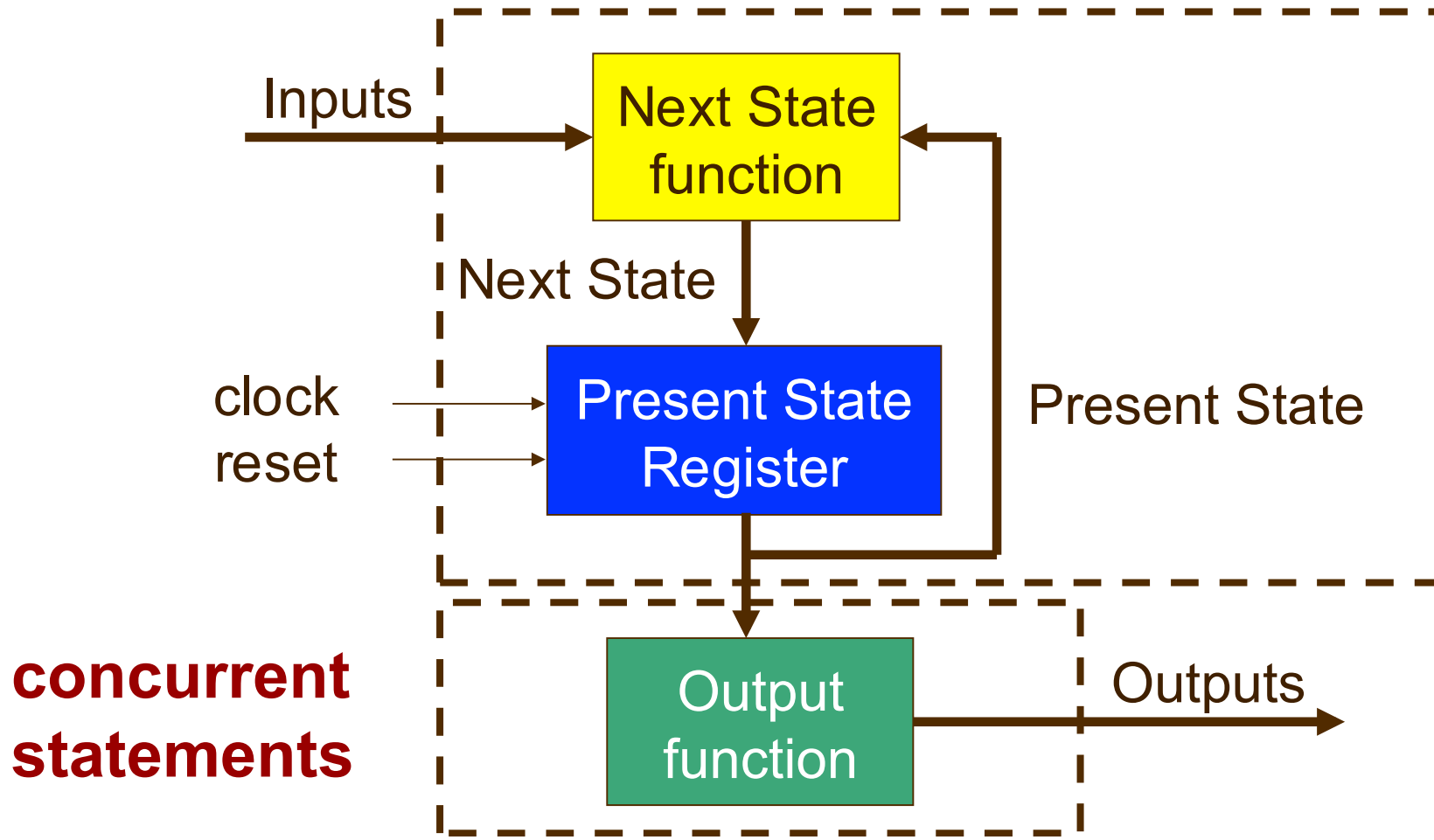

Mealy FSM


process(clock, reset)

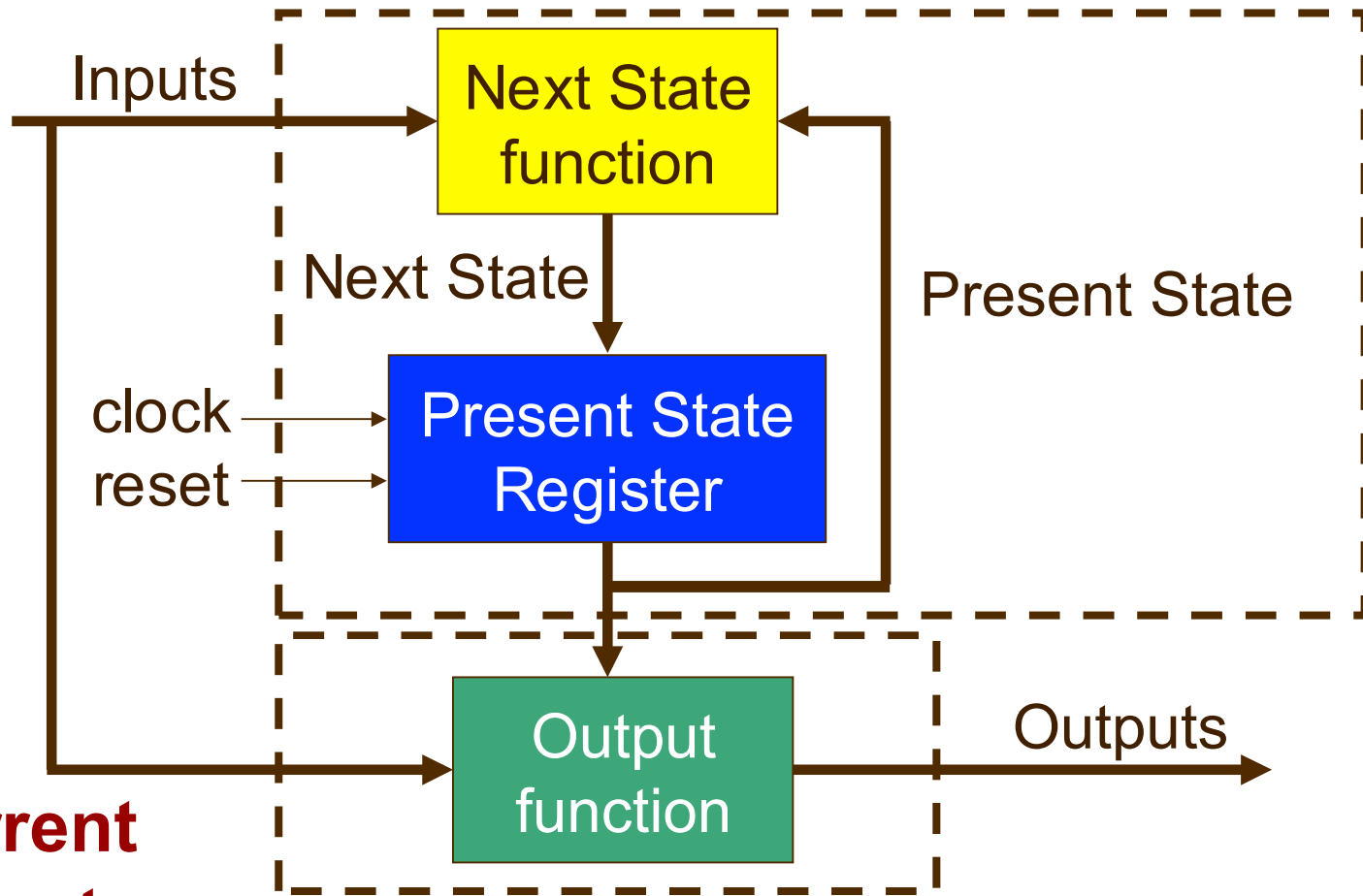

**concurrent
statements**

Moore FSM - Example 1

 - Moore FSM that Recognizes Sequence "10"



Moore FSM in VHDL (1)

```
TYPE state IS (S0, S1, S2);
```

```
SIGNAL Moore_state: state;
```

```
U_Moore: PROCESS (clock, reset)
```

```
BEGIN
```

```
    IF(reset = '1') THEN
```

```
        Moore_state <= S0;
```

```
    ELSIF (clock = '1' AND clock'event) THEN
```

```
        CASE Moore_state IS
```

```
            WHEN S0 =>
```

```
                IF input = '1' THEN
```

```
                    Moore_state <= S1;
```

```
                ELSE
```

```
                    Moore_state <= S0;
```

```
                END IF;
```


Moore FSM in VHDL (2)

```
    WHEN S1 =>
        IF input = '0' THEN
            Moore_state <= S2;
        ELSE
            Moore_state <= S1;
        END IF;
    WHEN S2 =>
        IF input = '0' THEN
            Moore_state <= S0;
        ELSE
            Moore_state <= S1;
        END IF;
    END CASE;
END IF;
END PROCESS;

Output <= '1' WHEN Moore_state = S2 ELSE '0';
```

Mealy FSM - Example 1

 - Mealy FSM that Recognizes Sequence “10”



Mealy FSM in VHDL (1)

```
TYPE state IS (S0, S1);  
SIGNAL Mealy_state: state;
```

```
U_Mealy: PROCESS(clock, reset)  
BEGIN
```

```
    IF(reset = '1') THEN
```

```
        Mealy_state <= S0;
```

```
    ELSIF (clock = '1' AND clock'event) THEN
```

```
        CASE Mealy_state IS
```

```
            WHEN S0 =>
```

```
                IF input = '1' THEN
```

```
                    Mealy_state <= S1;
```

```
                ELSE
```

```
                    Mealy_state <= S0;
```

```
                END IF;
```

Mealy FSM in VHDL (2)

```
        WHEN S1 =>
            IF input = '0' THEN
                Mealy_state <= S0;
            ELSE
                Mealy_state <= S1;
            END IF;
        END CASE;
    END IF;
END PROCESS;

Output <= '1' WHEN (Mealy_state = S1 AND input = '0') ELSE '0';
```