A central image of a Xilinx CoolRunner-II chip, a programmable logic device, with the Xilinx logo and 'CoolRunner-II' text on its surface.

**Algorithmic State Machine (ASM)  
Charts**

High Performance

coolClock

Low Power

coolClock


# Algorithmic State Machine

---


Algorithmic State Machine –  
representation of a Finite State Machine  
suitable for FSMs with a larger number of  
inputs and outputs compared to FSMs  
expressed using state diagrams and state  
tables.

# Elements used in ASM charts (1)


---

 

(a) State box

 

(b) Decision box

 


(c) Conditional output box
 
# State Box

---


- **State box** – represents a state.
- Equivalent to a node in a state diagram or a row in a state table.
- Contains register transfer actions or output signals
- **Moore-type outputs are listed inside of the box.**
- It is customary to write only the name of the signal that has to be asserted in the given state, e.g.,  $z$  instead of  $z \leq 1$ .
- Also, it might be useful to write an action to be taken, e.g.,  $\text{count} \leq \text{count} + 1$ , and only later translate it to asserting a control signal that causes a given action to take place (e.g., enable signal of a counter).


 
# Decision Box

---


- **Decision box** – indicates that a given condition is to be tested and the exit path is to be chosen accordingly. The condition expression may include one or more inputs to the FSM.


 
# Conditional Output Box

---

- **Conditional output box**
- **Denotes output signals that are of the Mealy type.**
- The condition that determines whether such outputs are generated is specified in the decision box.




# ASMs representing simple FSMs

---

- Algorithmic state machines can model both Mealy and Moore Finite State Machines
- They can also model machines that are of the mixed type

# Moore FSM – Example 2: State diagram

---

 




# Moore FSM – Example 2: State table

---

| Present state | Next state |         | Output $z$ |
|---------------|------------|---------|------------|
|               | $w = 0$    | $w = 1$ |            |
| A             | A          | B       | 0          |
| B             | A          | C       | 0          |
| C             | A          | C       | 1          |

# ASM Chart for Moore FSM – Example 2

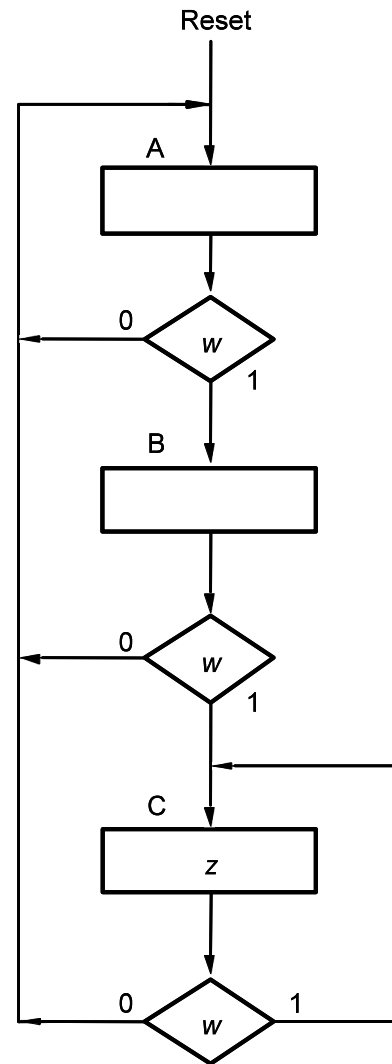

# Example 2: VHDL code (1)

---

```
USE ieee.std_logic_1164.all ;
```

```
ENTITY simple IS
```

```
    PORT ( clock  : IN STD_LOGIC ;  
          resetn  : IN STD_LOGIC ;  
          w       : IN STD_LOGIC ;  
          z       : OUT STD_LOGIC ) ;
```

```
END simple ;
```

```
ARCHITECTURE Behavior OF simple IS
```

```
    TYPE State_type IS (A, B, C) ;  
    SIGNAL y : State_type ;
```

```
BEGIN
```

```
    PROCESS ( resetn, clock )  
    BEGIN
```

```
        IF resetn = '0' THEN
```

```
            y <= A ;
```

```
        ELSIF (Clock'EVENT AND Clock = '1') THEN
```

## Example 2: VHDL code (2)

---

```
CASE y IS
  WHEN A =>
    IF w = '0' THEN
      y <= A ;
    ELSE
      y <= B ;
    END IF ;
  WHEN B =>
    IF w = '0' THEN
      y <= A ;
    ELSE
      y <= C ;
    END IF ;
  WHEN C =>
    IF w = '0' THEN
      y <= A ;
    ELSE
      y <= C ;
    END IF ;
END CASE ;
```

---

## Example 2: VHDL code (3)

---


```
    END IF ;  
END PROCESS ;
```

```
z <= '1' WHEN y = C ELSE '0' ;
```


```
END Behavior ;
```

# Mealy FSM – Example 3: State diagram

---

 

# ASM Chart for Mealy FSM – Example 3

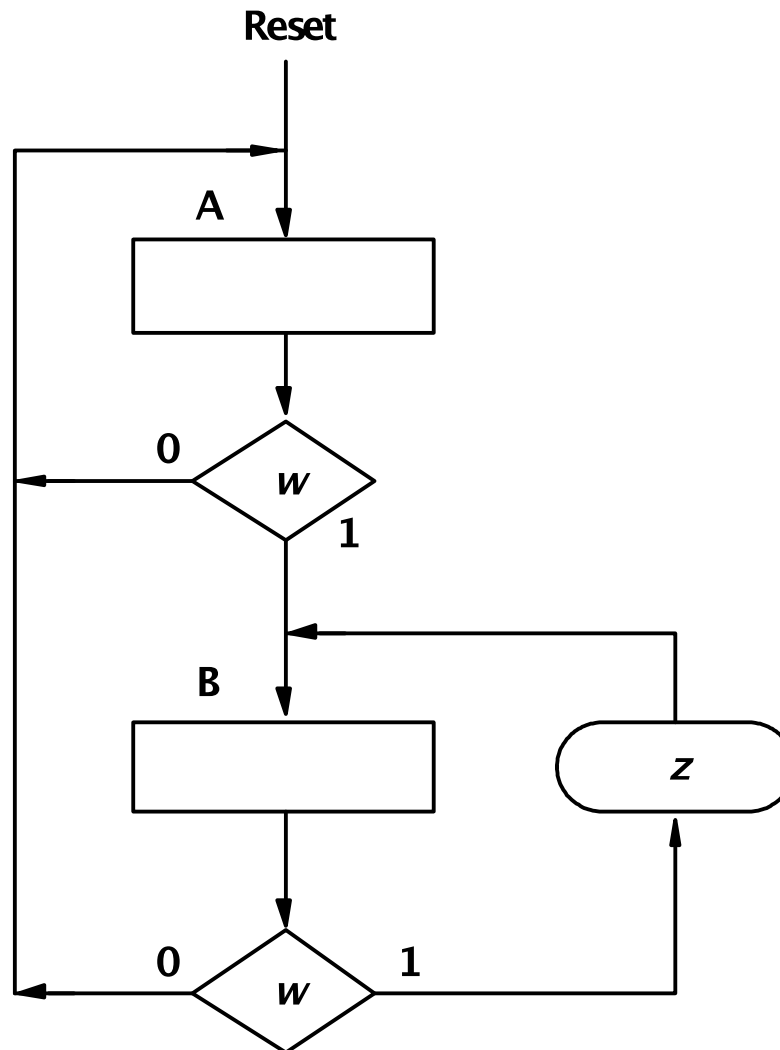

# Example 3: VHDL code (1)

---

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY Mealy IS
    PORT ( clock      : IN      STD_LOGIC ;
          resetn     : IN      STD_LOGIC ;
          w          : IN      STD_LOGIC ;
          z          : OUT     STD_LOGIC ) ;
END Mealy ;

ARCHITECTURE Behavior OF Mealy IS
    TYPE State_type IS (A, B) ;
    SIGNAL y : State_type ;
BEGIN
    PROCESS ( resetn, clock )
    BEGIN
        IF resetn = '0' THEN
            y <= A ;
        ELSIF (clock'EVENT AND clock = '1') THEN
```



# Example 3: VHDL code (2)

---

```
CASE y IS
  WHEN A =>
    IF w = '0' THEN
      y <= A ;
    ELSE
      y <= B ;
    END IF ;
  WHEN B =>
    IF w = '0' THEN
      y <= A ;
    ELSE
      y <= B ;
    END IF ;
END CASE ;
```

# Example 3: VHDL code (3)

---


```
    END IF ;  
END PROCESS ;
```

```
z <= '1' WHEN (y = B) AND (w='1') ELSE '0' ;
```


```
END Behavior ;
```

# Control Unit Example: Arbiter (1)


---

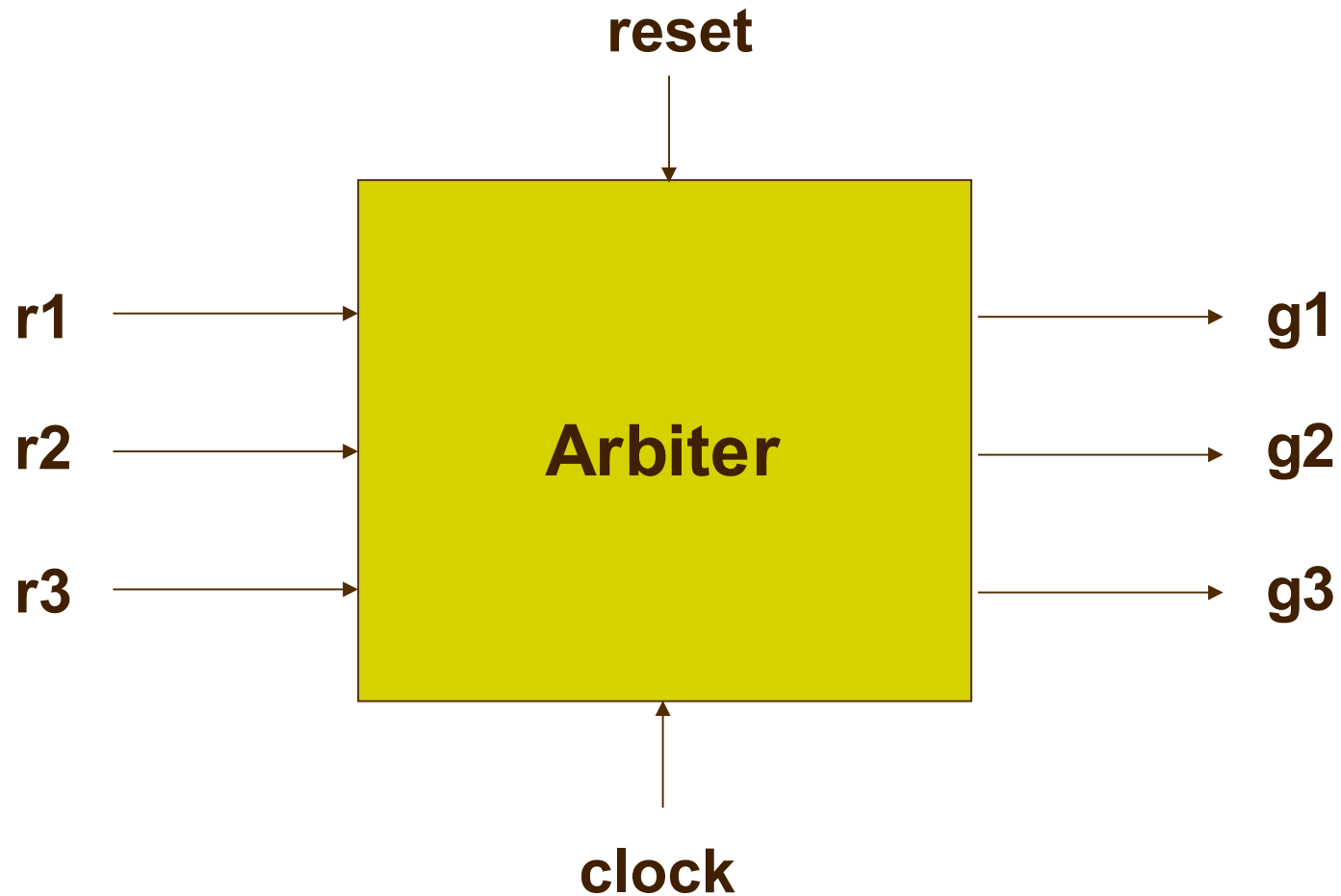


# Control Unit Example: Arbiter (2)

 

# Control Unit Example: Arbiter (3)

 

# ASM Chart for Control Unit - Example 4

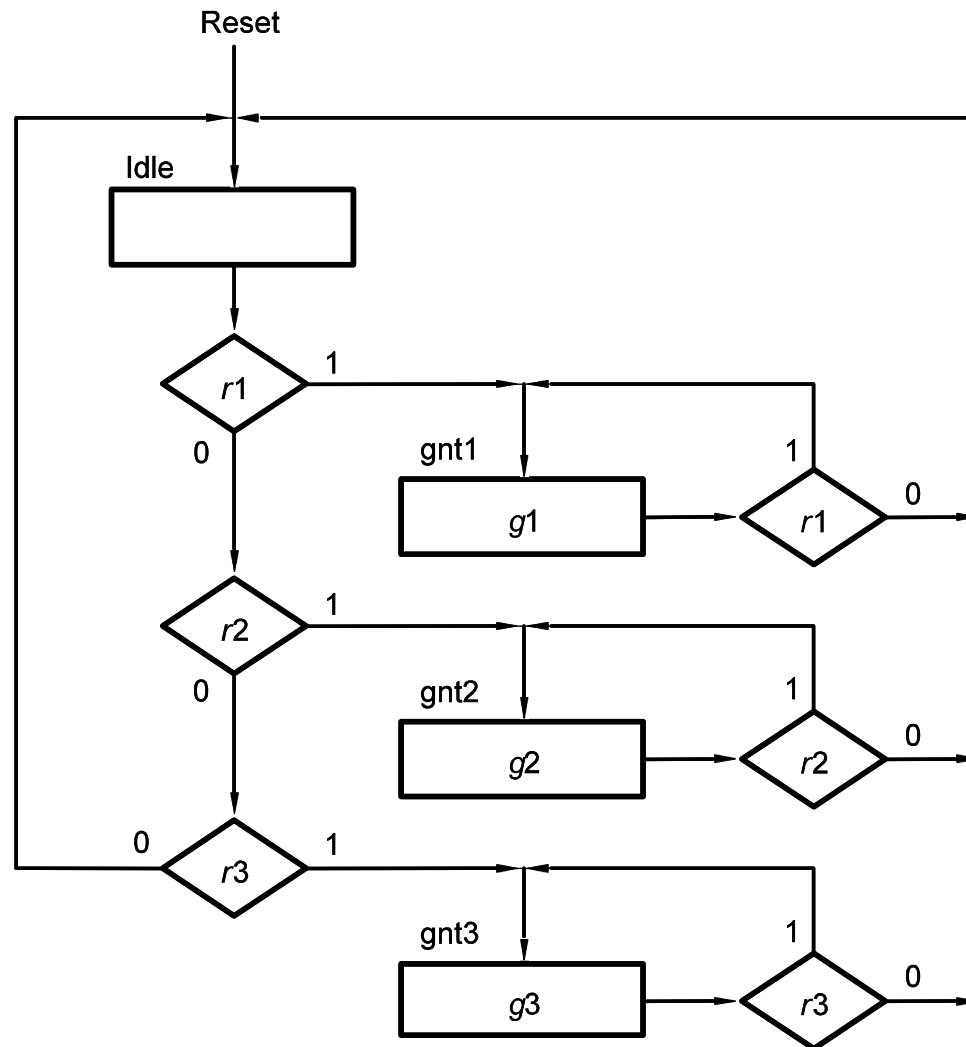

# Example 4: VHDL code (1)

---

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY arbiter IS
    PORT ( Clock, Resetn : IN      STD_LOGIC ;
          r               : IN      STD_LOGIC_VECTOR(1 TO 3) ;
          g               : OUT     STD_LOGIC_VECTOR(1 TO 3) ) ;
END arbiter ;

ARCHITECTURE Behavior OF arbiter IS
    TYPE State_type IS (Idle, gnt1, gnt2, gnt3) ;
    SIGNAL y : State_type ;
```

# Example 4: VHDL code (2)

---

```
BEGIN
  PROCESS ( Resetn, Clock )
  BEGIN
    IF Resetn = '0' THEN y <= Idle ;
    ELSIF (Clock'EVENT AND Clock = '1') THEN
      CASE y IS
        WHEN Idle =>
          IF r(1) = '1' THEN y <= gnt1 ;
          ELSIF r(2) = '1' THEN y <= gnt2 ;
          ELSIF r(3) = '1' THEN y <= gnt3 ;
          ELSE y <= Idle ;
          END IF ;
        WHEN gnt1 =>
          IF r(1) = '1' THEN y <= gnt1 ;
          ELSE y <= Idle ;
          END IF ;
        WHEN gnt2 =>
          IF r(2) = '1' THEN y <= gnt2 ;
          ELSE y <= Idle ;
          END IF ;
```



# Example 4: VHDL code (3)

---

```
                WHEN gnt3 =>
                    IF r(3) = '1' THEN y <= gnt3 ;
                    ELSE y <= Idle ;
                    END IF ;
                END CASE ;
            END IF ;
        END PROCESS ;

g(1) <= '1' WHEN y = gnt1 ELSE '0' ;
g(2) <= '1' WHEN y = gnt2 ELSE '0' ;
g(3) <= '1' WHEN y = gnt3 ELSE '0' ;
END Behavior ;
```