



**Centurion**  
**UNIVERSITY**

*Shaping Lives...*  
*Empowering Communities...*

# Advanced RTL Simulation



Centurion  
UNIVERSITY

*Shaping Lives  
Empowering Communities...*

# Abstract

RTL simulations do not consider timing in all aspects and therefore, the results produced by simulation may differ from silicon behavior. Simulation can miss design bugs due to limitations in simulator. These differences are due to incorrect estimation of propagation time between clock and data paths causing data to propagate earlier than in silicon. This problem is known as shoot-thru.

We faced a silicon failure which prompted us to understand how shoot-thru situations occur during simulation, identify these situations with higher accuracy of analysis and fix them with minimal impact using simple RTL coding rules.

We teamed up with Atrenta to automate efficiently the check of those coding rules.




Centurion  
UNIVERSITY  
Shaping Lives  
Empowering Communities
 
# What is Shoot-thru?

When any signal jumps over an *extra* register within one clock cycle.

E.g. Input “din” crosses 2 register within one clock cycle.




**Shoot-thru:**

**(events in data path) <= (events in clock path)**





**Centurion**  
**UNIVERSITY**  
Shaping Lives...  
Empowering Communities...

# How Simulation Shoot-thru occurs?

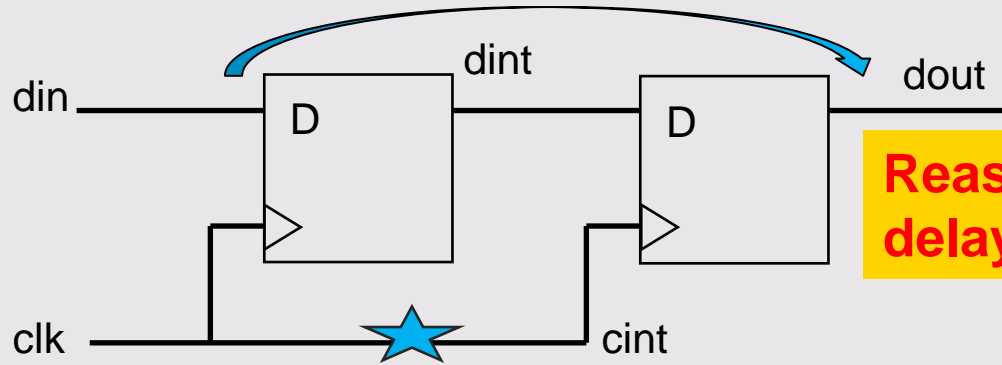

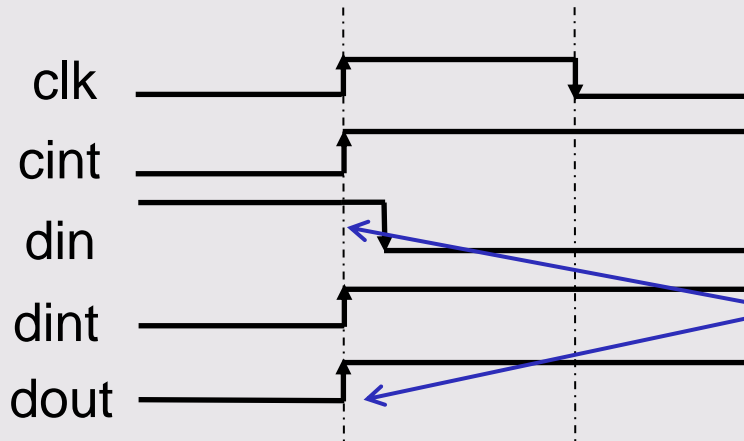 **Reason : Extra Delta delay in Clock Path**



**Consequence : "dout" same as "din" within single clock**




Centurion  
UNIVERSITY

Shaping Lives...  
Empowering Communities...

# Will Verilog coding rules help?

blocking assignment in  
combination blocks and  
non-blocking in sequential

*Not, always safe....*

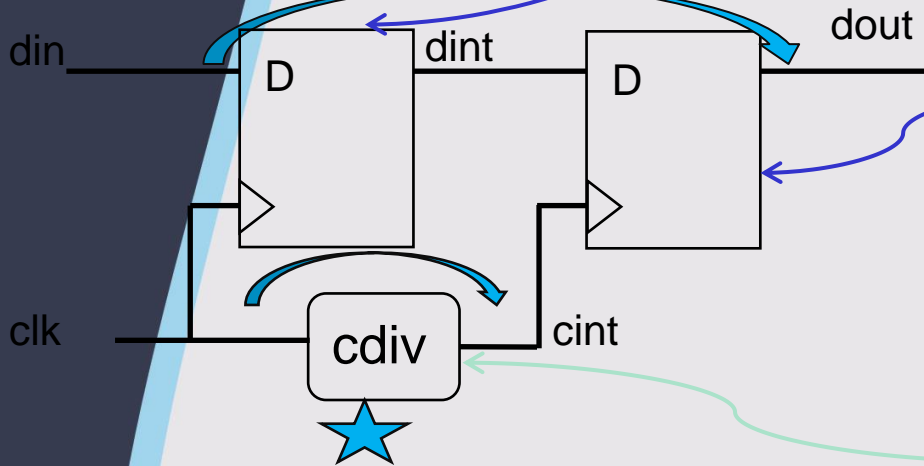

## // Input data sampling

```
always @ (posedge clk, negedge rst_n) begin
    if (rst_n==1'b0)
        dint <= din;
    else
        dint <= din;
end
```

## // Capture data on divided clock

```
always @ (posedge cint, negedge rst_n) begin
    if (rst_n==1'b0)
        dout <= 1'b0;
    else
        dout <= dint;
end
```

## // Sequential clock generation

```
always @ (posedge clk, negedge rst_n) begin
    if (rst_n==1'b0)
        cint <= 1'b0;
    else
        cint <= !cint;
end
```

**Extra Delta-delay in Clock Path**

**Non-blocking assignments consume *delta* delay**




# Case 1: Verification can miss Shoot-thru

- User specification was to transfer “din” to “dout” in 1 cycle
- Extra flop was a mistake but not caught by RTL verification.

Centurion  
UNIVERSITY  
Shaping Lives...  
Empowering Communities...

 *If Simulation has shoot-thru => “din” will be captured at “dout” in 1 cycle  
=> All tests pass as per user specification*



*Silicon fails as “din” will be captured at “dout” in 2 cycles  
=> one cycle extra delay vs. Specification*


- Existence of One extra flop causes silicon failure.




**Centurion**  
**UNIVERSITY**  
Shaping Lives...  
Empowering Communities...
 
# Case 2: Verification can miss Shoot-thru


- User specification was to transfer “din” to “dout” in 2 cycle
- However, shoot-thru may cause simulation failure
- User fixes it by adding an extra flop



*Simulation Fails*

 

*Simulation Passes after rtl changes*

 


*Silicon Fails*



**Centurion**  
**UNIVERSITY**  
*Shaping Lives...  
Empowering Communities...*

# Potential Gap in design flow

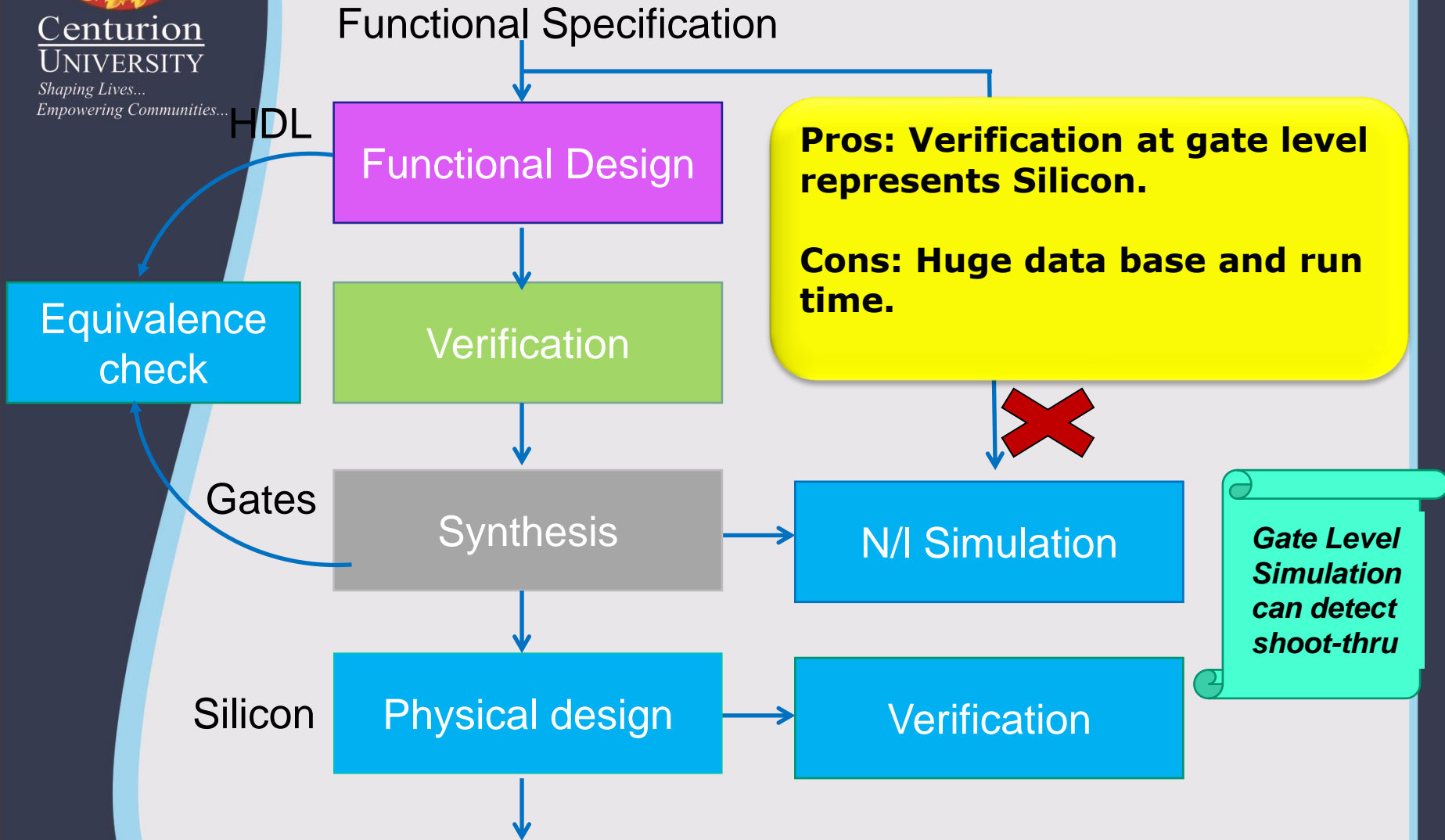




# So, How to detect shoot-thru issues?

By using an improved simulator?

UNIVERSITY

Shaping Lives  
Empowering Communities...

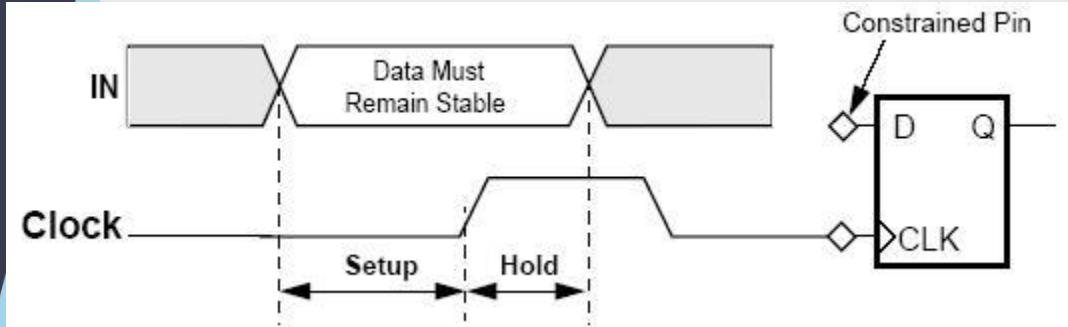**NO**, as root cause of problem is that RTL Simulation has no notion of timing delay & Hold checks.



By doing Gate level simulation?

**Yes** but it is very costly.

By using robust RTL coding rules?

**Yes!** this is easy and efficient (see subsequent slides)



Centurion  
UNIVERSITY  
Shaping Lives...  
Empowering Communities...

# Rule 1 - Force scheduling of data

Force physical time delay in Sequential data assignments

10


Signal is delayed in 'physical time', instead of 'delta' time.

Verilog

```
dint <= #1 din ;
```

VHDL

```
dint <= din after 1 ns;
```

 

**This adds an extra delay in data path**




Centurion  
UNIVERSITY

Shaping Lives...  
Empowering Communities...

# Rule 2 - No 'physical delay' in clock path

11

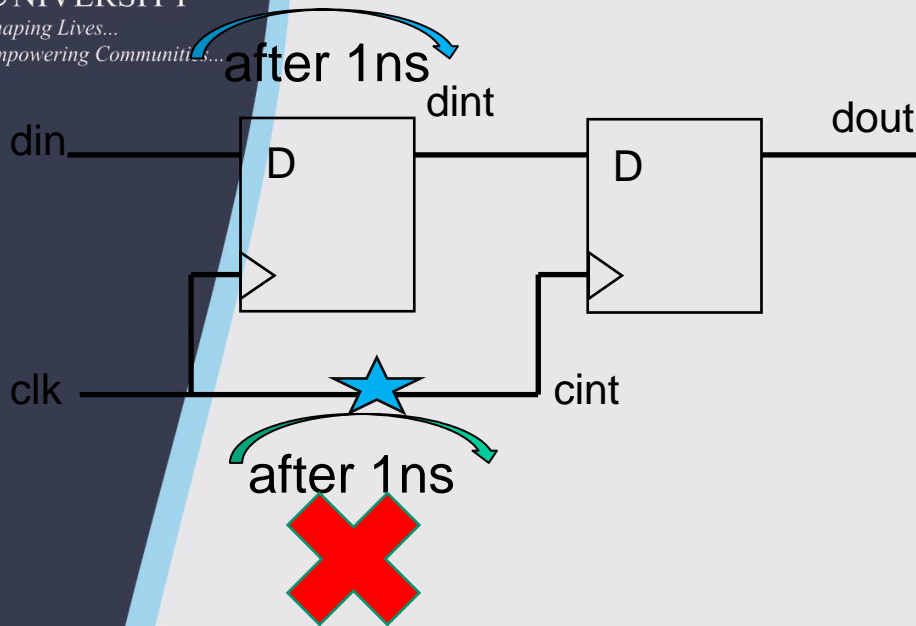

Delay on clock paths competes with delay on Data path

Clock vs Data scheduling still un-reliable


**No unwanted delay on clock path**

**Rule1 + Rule2 ensures no risk of shoot-thru  
i.e data is updated after clock**



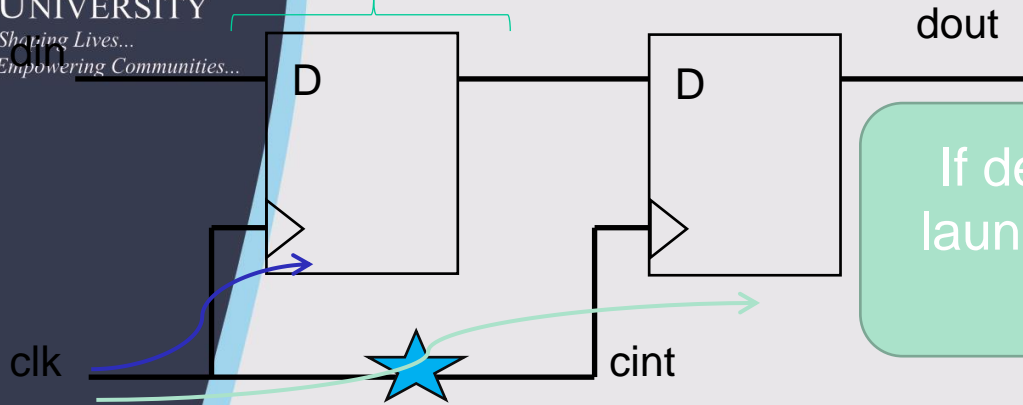
# Automation with SpyGlass RTL checker

Rule 1 – Reports missing needed delay in data path



If delta delay is different between launch and capture flop, add delay on launch flop

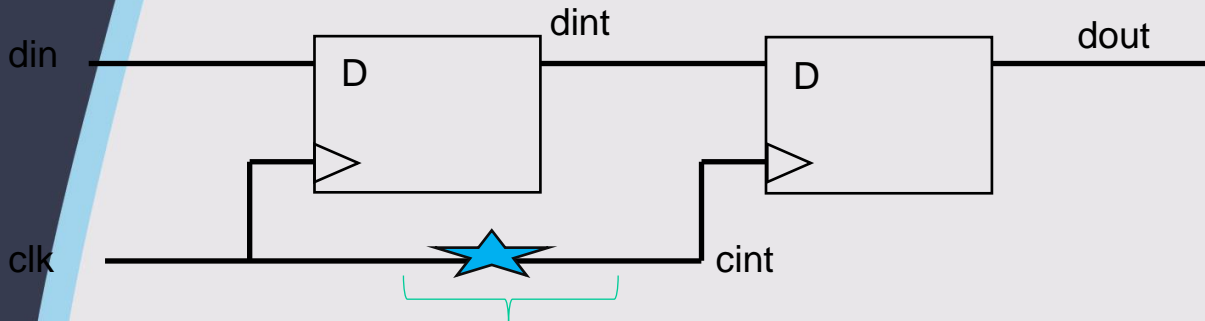

Rule 2 – Reports extra delay (Physical) present in clock path

**Easy to identify shoot-thru prone RTL**




Centurion  
UNIVERSITY

Shaping Lives...  
Empowering Communities...


# Checker catches Real Silicon Issues

Missing delay was causing silicon failure

13

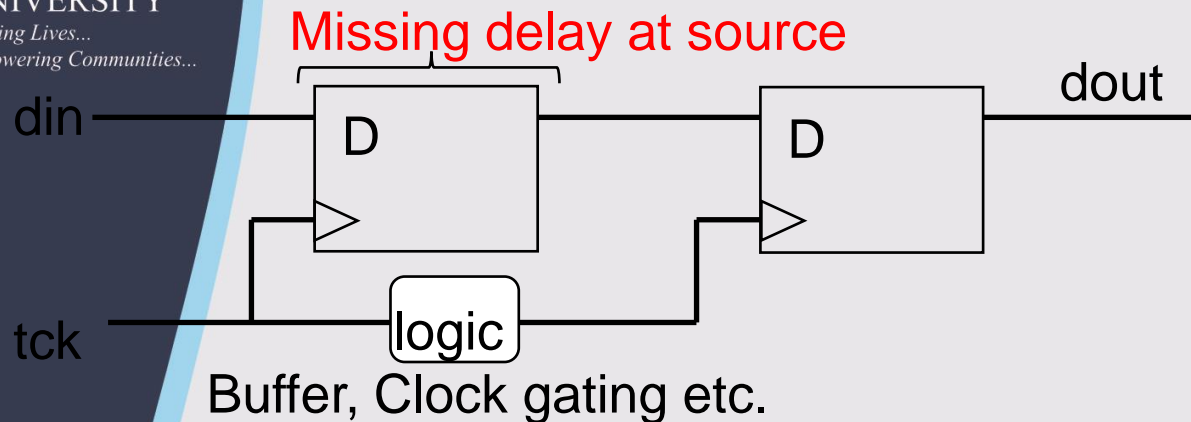

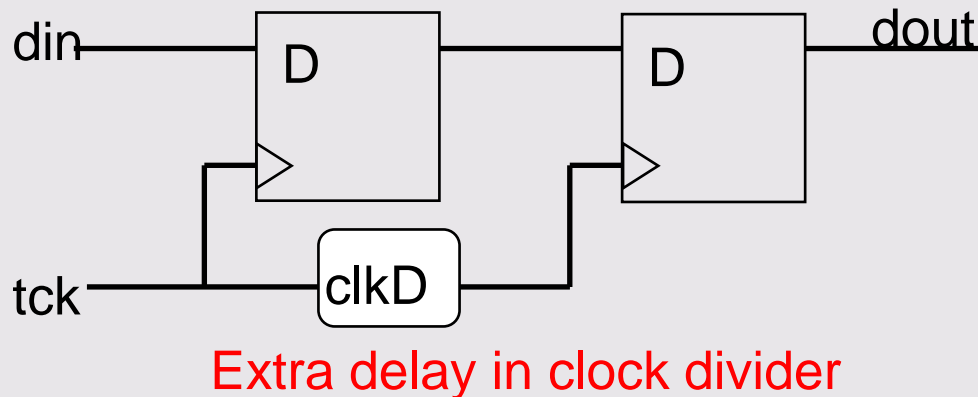- Unintentional delay in clock path found on another chip
  - User specified physical delay on source flop - Still problem occurred due to physical delay specified on clock path





Centurion  
UNIVERSITY

Shaping Lives  
Empowering Communities

# Conclusion

Simulators create events and schedule them, but with no notion of timing checks across data and clock events

Shoot-thru impacts RTL Simulation and may cause false simulation behavior, masking the real issues

Simple RTL coding rules can prevent the problem to occur

- Possibly add physical delays on data path to force scheduling

- Avoid physical delays on clock path

Spyglass RTL checker can help you to efficiently check those rules and removes need of costly gate level simulations.

## Next Steps

- Extend the SpyGlass checks to ensure that every output interface is having delayed assignment