

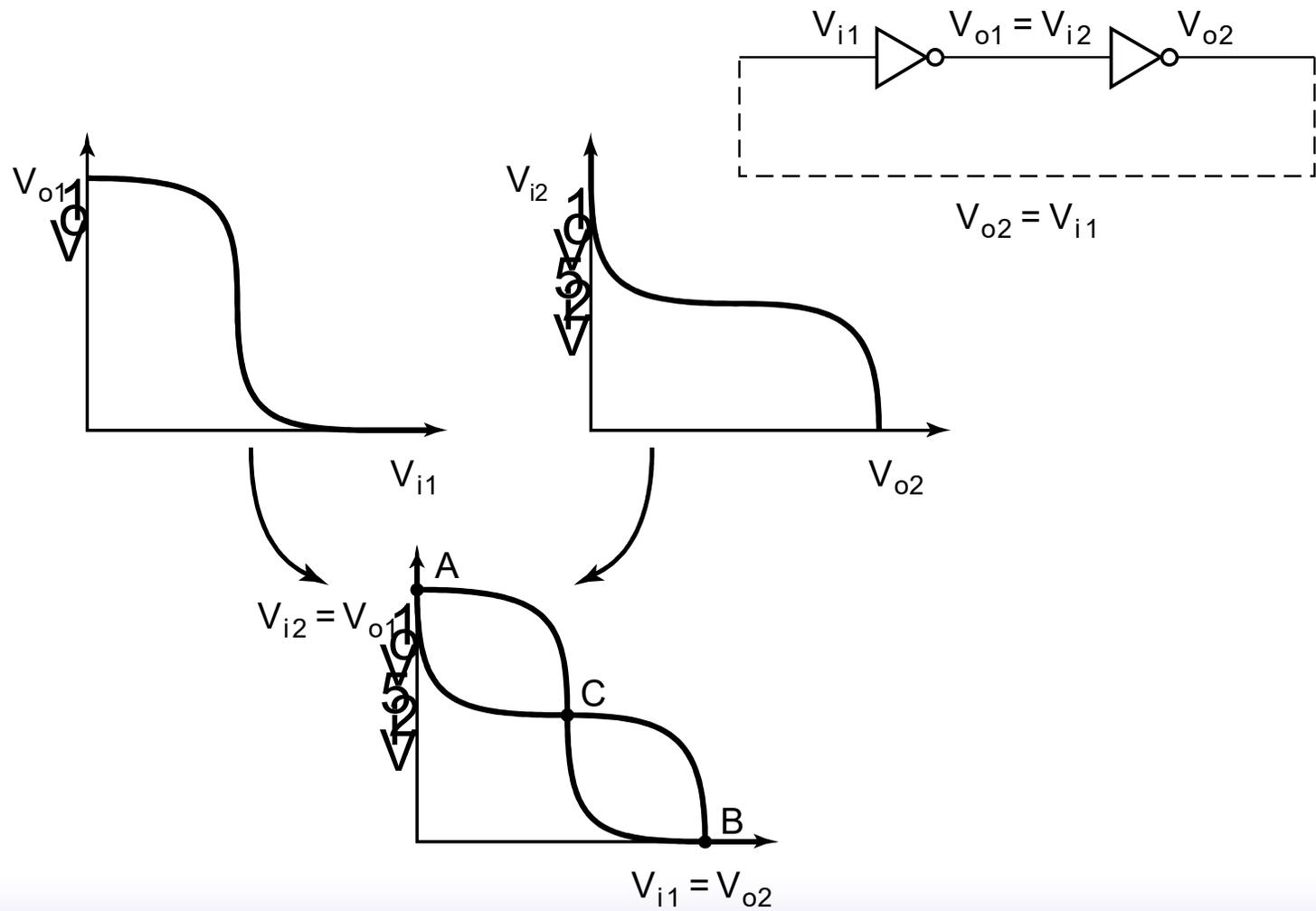


# Positive Feedback: Bi-Stability

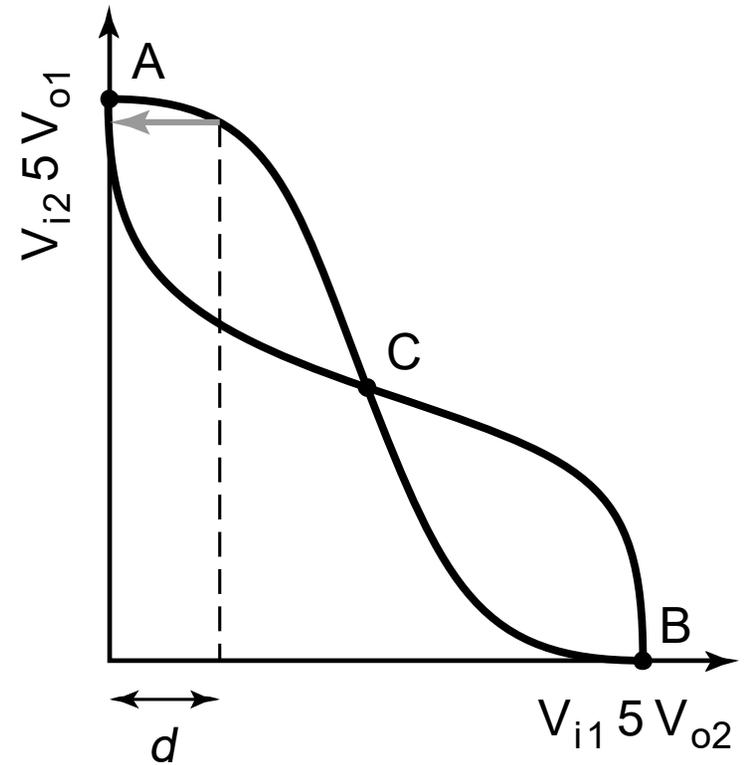


# Meta-Stability

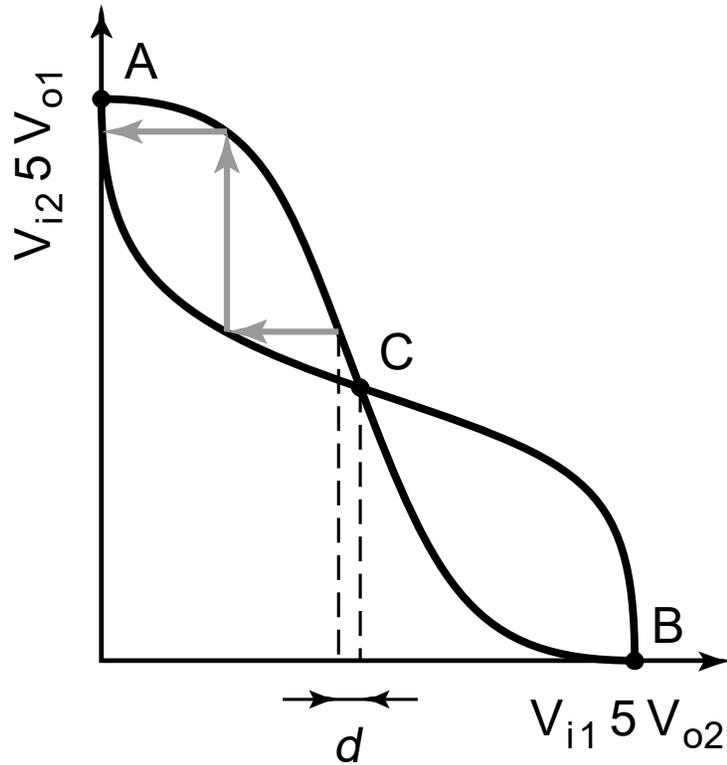


**Gain should be larger than 1 in the transition region**
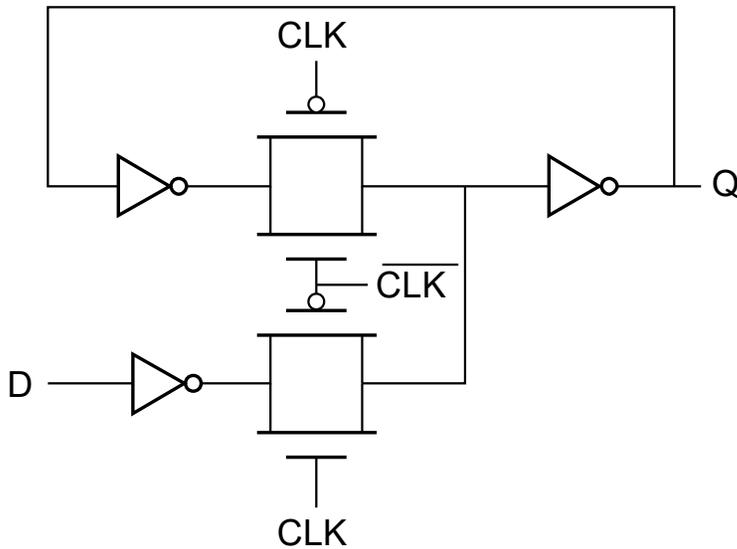
# Writing into a Static Latch

Use the clock as a decoupling signal, that distinguishes between the transparent and opaque states




Converting into a MUX

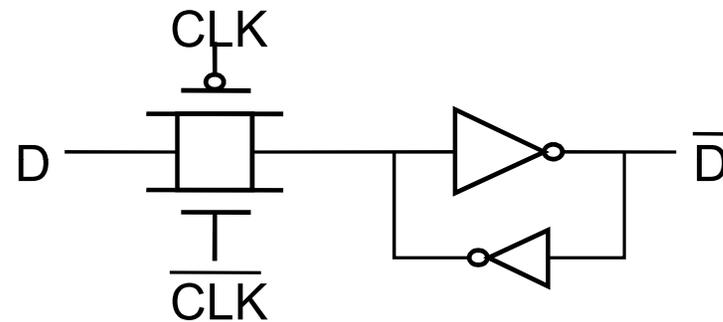

Forcing the state  
(can implement as NMOS-only)

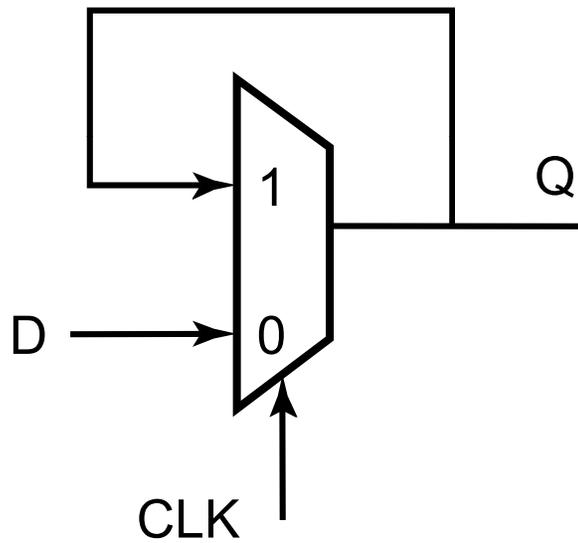
# Mux-Based Latches

Negative latch  
(transparent when CLK= 0)




$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$

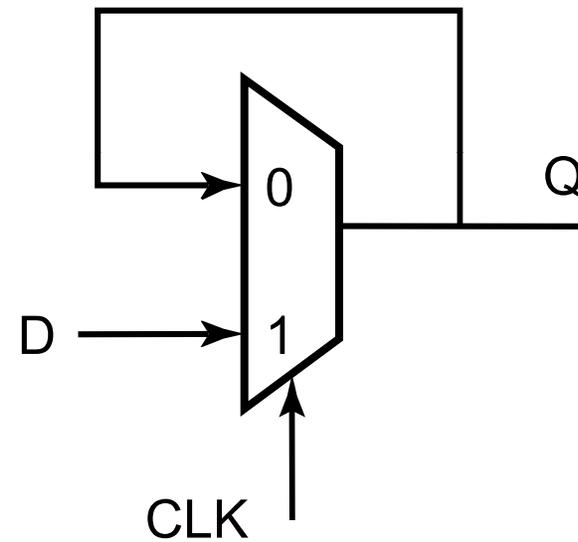Positive latch  
(transparent when CLK= 1)




$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$


# Mux-Based Latch

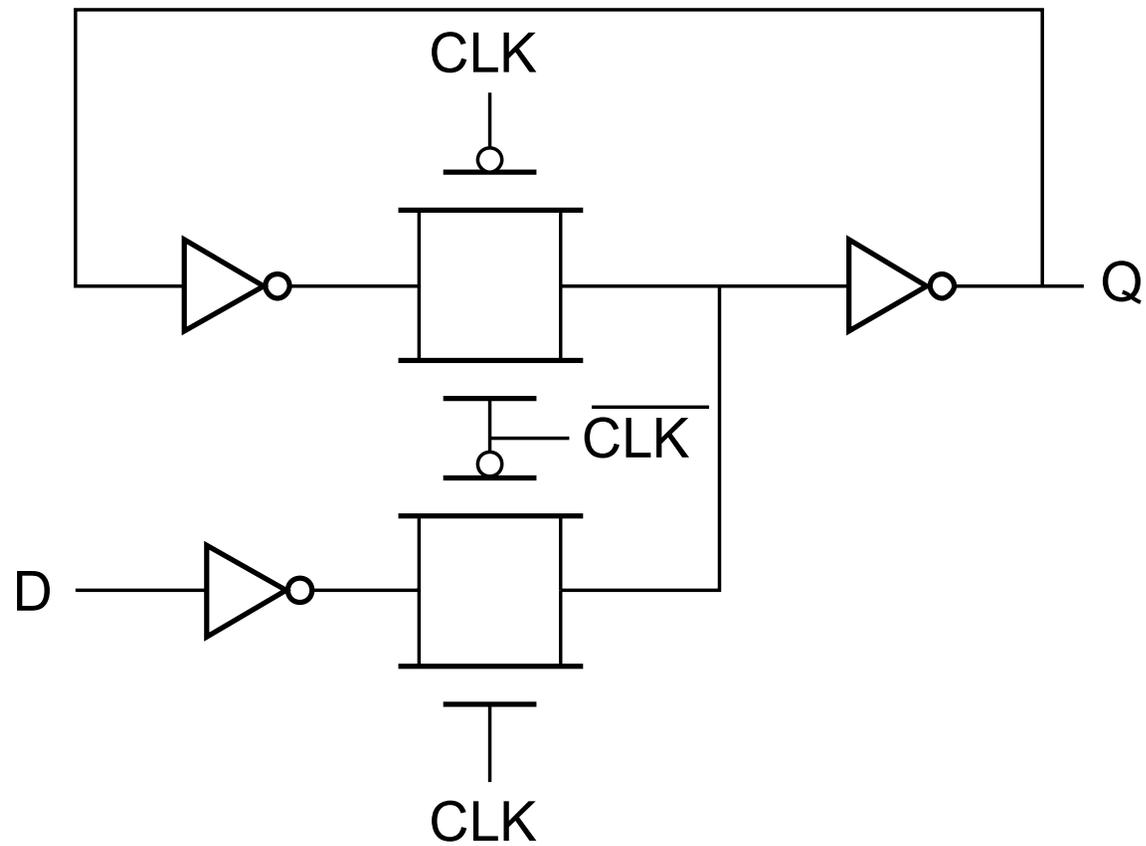

# Mux-Based Latch

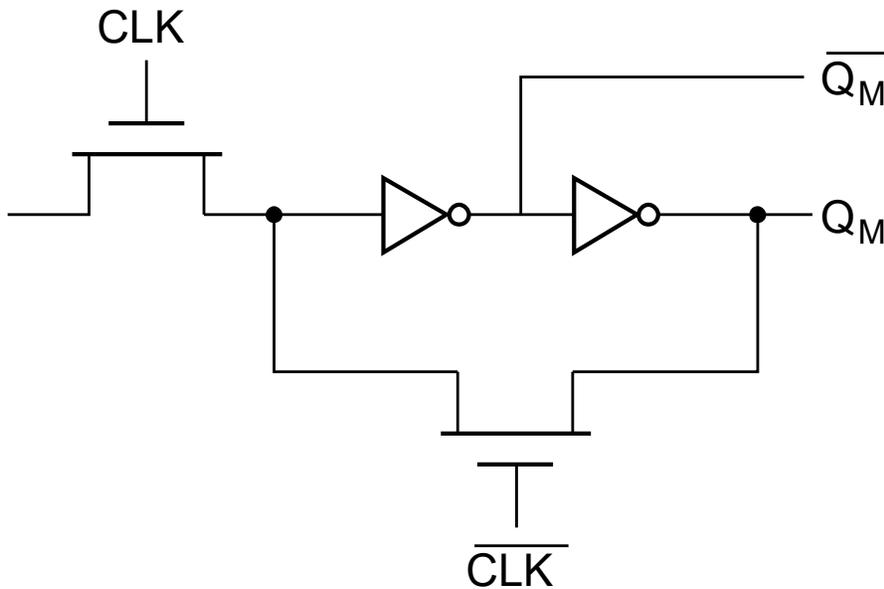

NMOS only

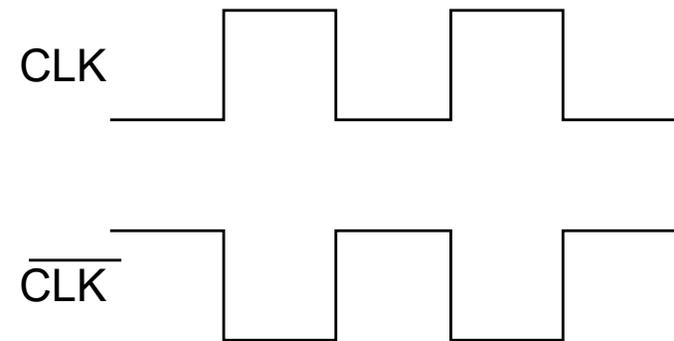

Non-overlapping clocks