

# *Read-Write Memories (RAM)*

## □ **STATIC (SRAM)**

**Data stored as long as supply is applied**

**Large (6 transistors/cell)**

**Fast**

**Differential**

## □ **DYNAMIC (DRAM)**

**Periodic refresh required**


**Small (1-3 transistors/cell)**

**Slower**

**Single Ended**




# CMOS SRAM Analysis (Read)

 

$$k_{n,M5} \left( (V_{DD} - \Delta V - V_{Tn}) V_{DSATn} - \frac{V_{DSATn}^2}{2} \right) = k_{n,M1} \left( (V_{DD} - V_{Tn}) \Delta V - \frac{\Delta V^2}{2} \right)$$


$$\Delta V = \frac{V_{DSATn} + CR(V_{DD} - V_{Tn}) - \sqrt{V_{DSATn}^2(1 + CR) + CR^2(V_{DD} - V_{Tn})^2}}{CR}$$

# CMOS SRAM Analysis (Read)

 

$$CR = \frac{W_1/L_1}{W_5/L_5}$$


# CMOS SRAM Analysis (Write)

 


$$k_{n, M6} \left( (V_{DD} - V_{Tn}) V_Q - \frac{V_Q^2}{2} \right) = k_{p, M4} \left( (V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)$$

$$V_Q = V_{DD} - V_{Tn} - \sqrt{(V_{DD} - V_{Tn})^2 - 2 \frac{\mu_p}{\mu_n} PR \left( (V_{DD} - |V_{Tp}|) V_{DSATp} - \frac{V_{DSATp}^2}{2} \right)},$$


# CMOS SRAM Analysis (Write)

 

# 6T-SRAM — Layout

 

# Resistance-load SRAM Cell

 

Static power dissipation -- Want  $R_L$  large  
Bit lines precharged to  $V_{DD}$  to address  $t_p$  problem

# SRAM Characteristics

**Table 12-2** Comparison of CMOS SRAM cells used in 1-Mbit memory (from [Takada91])

	<b>Complementary CMOS</b>	<b>Resistive Load</b>	<b>TFT Cell</b>
Number of transistors	6	4	4 (+2 TFT)
Cell size	58.2 $\mu\text{m}^2$ (0.7- $\mu\text{m}$ rule)	40.8 $\mu\text{m}^2$ (0.7- $\mu\text{m}$ rule)	41.1 $\mu\text{m}^2$ (0.8- $\mu\text{m}$ rule)
Standby current (per cell)	$10^{-15}$ A	$10^{-12}$ A	$10^{-13}$ A