 


3-Transistor DRAM Cell




No constraints on device ratios


Reads are non-destructive

Value stored at node X when writing a "1" = $V_{WWL} - V_{Tn}$

3T-DRAM — Layout

 

1-Transistor DRAM Cell

 

Write: C_S is charged or discharged by asserting WL and BL.

Read: Charge redistribution takes places between bit line and storage capacitance


$$\Delta V = V_{BL} - V_{PRE} = V_{BIT} - V_{PRE} \frac{C_S}{C_S + C_{BL}}$$

Voltage swing is small; typically around 250 mV.


DRAM Cell Observations

- ❑ 1T DRAM requires a sense amplifier for each bit line, due to charge redistribution read-out.
- ❑ DRAM memory cells are single ended in contrast to SRAM cells.
- ❑ The read-out of the 1T DRAM cell is destructive; read and refresh operations are necessary for correct operation.
- ❑ Unlike 3T cell, 1T cell requires presence of an extra capacitance that must be explicitly included in the design.
- ❑ When writing a “1” into a DRAM cell, a threshold voltage is lost. This charge loss can be circumvented by bootstrapping the word lines to a higher value than V_{DD}


Sense Amp Operation

 

1-T DRAM Cell

 

Cross-section

 


Layout


Uses Polysilicon-Diffusion Capacitance

Expensive in Area


SEM of poly-diffusion capacitor 1T-DRAM

 

Advanced 1T DRAM Cells

 

Trench Cell

 

Stacked-capacitor Cell